



دانشگاه صنعتی امیر کبیر
(پلی تکنیک تهران)

Electrical and Electronic Circuits

chapter 13. Operational Amplifier

Afarghadan@aut.ac.ir

عظیم فرقدان 



مهر ۱۴۰۳

Objectives of the Lecture


- Introduction to Operational Amplifiers
 - Precise Model of Operational Amplifiers
 - Ideal Model
 - Applications of Operational Amplifiers
 - Inverting Amplifier
 - Non-Inverting Amplifier
 - Voltage Follower (Buffer)
 - Multi-Stage Amplifier
 - Ideal Voltage and Current Sources
- Comparator Circuit
- Several Examples

Operational Amplifier (Op-Amp)

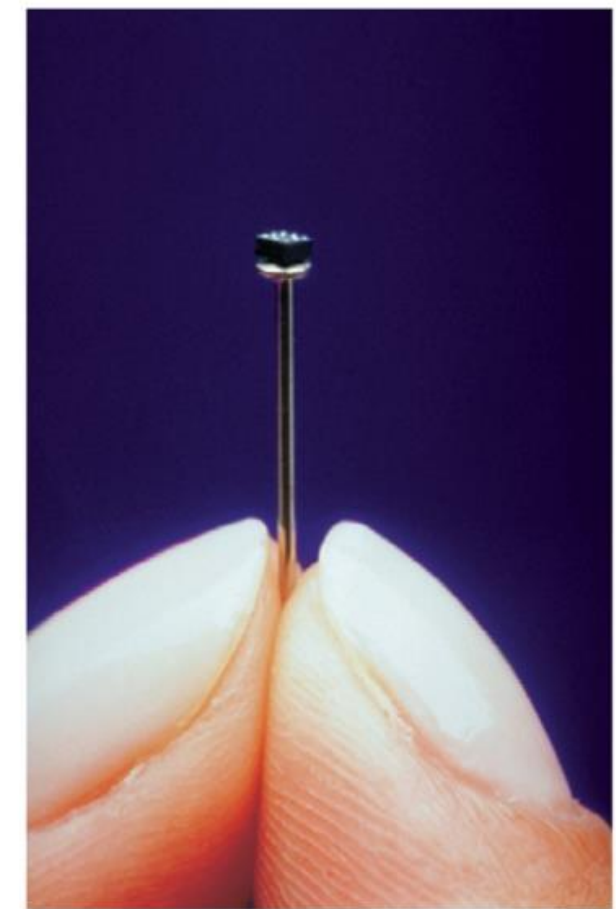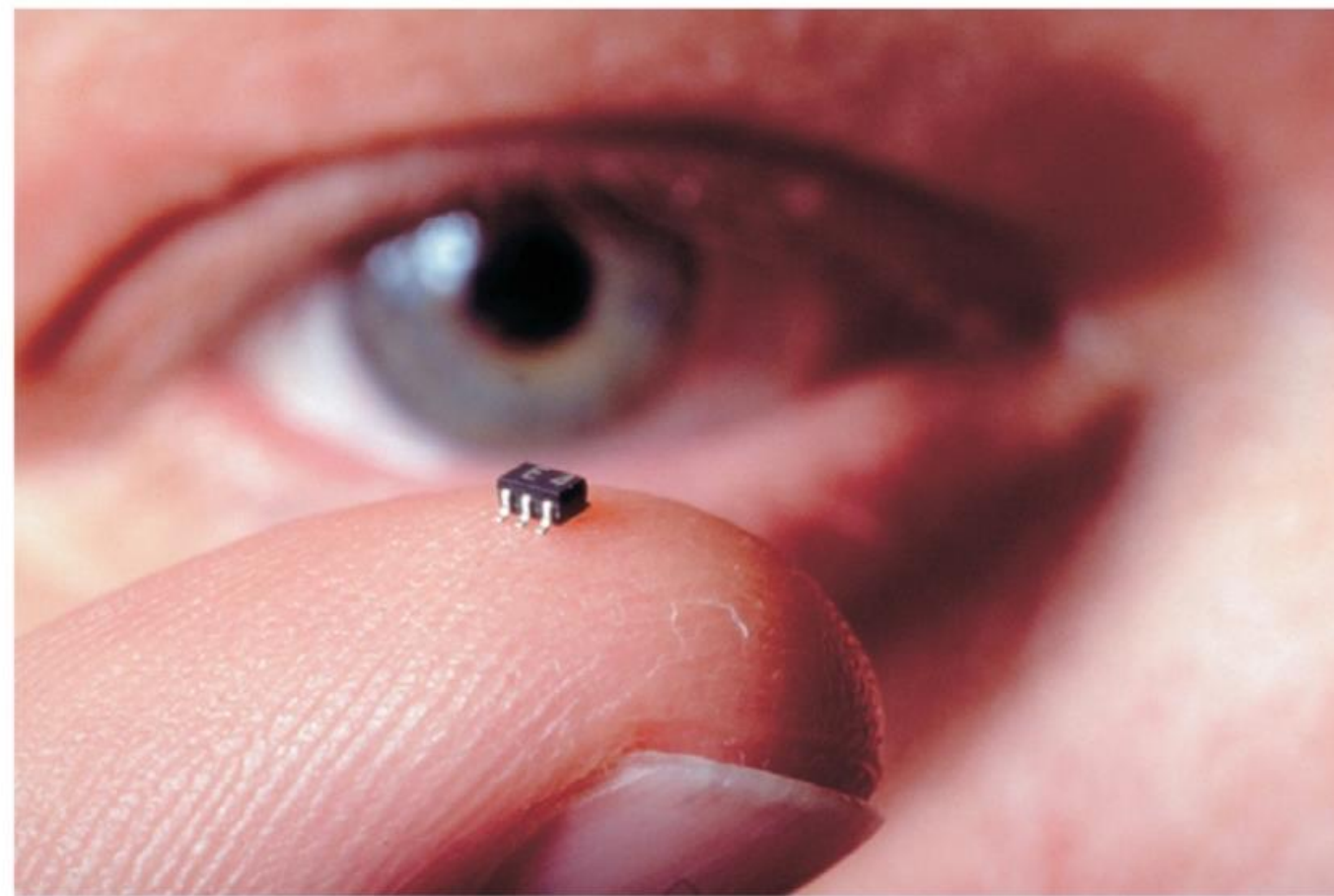
- The **Operational Amplifier (Op-Amp)** is an integrated circuit (IC) widely utilized as an amplifier in various applications.
- Its origins date back to the 1940s when it was employed in analog computational circuits for constructing adders, sub tractors, and analog multipliers.



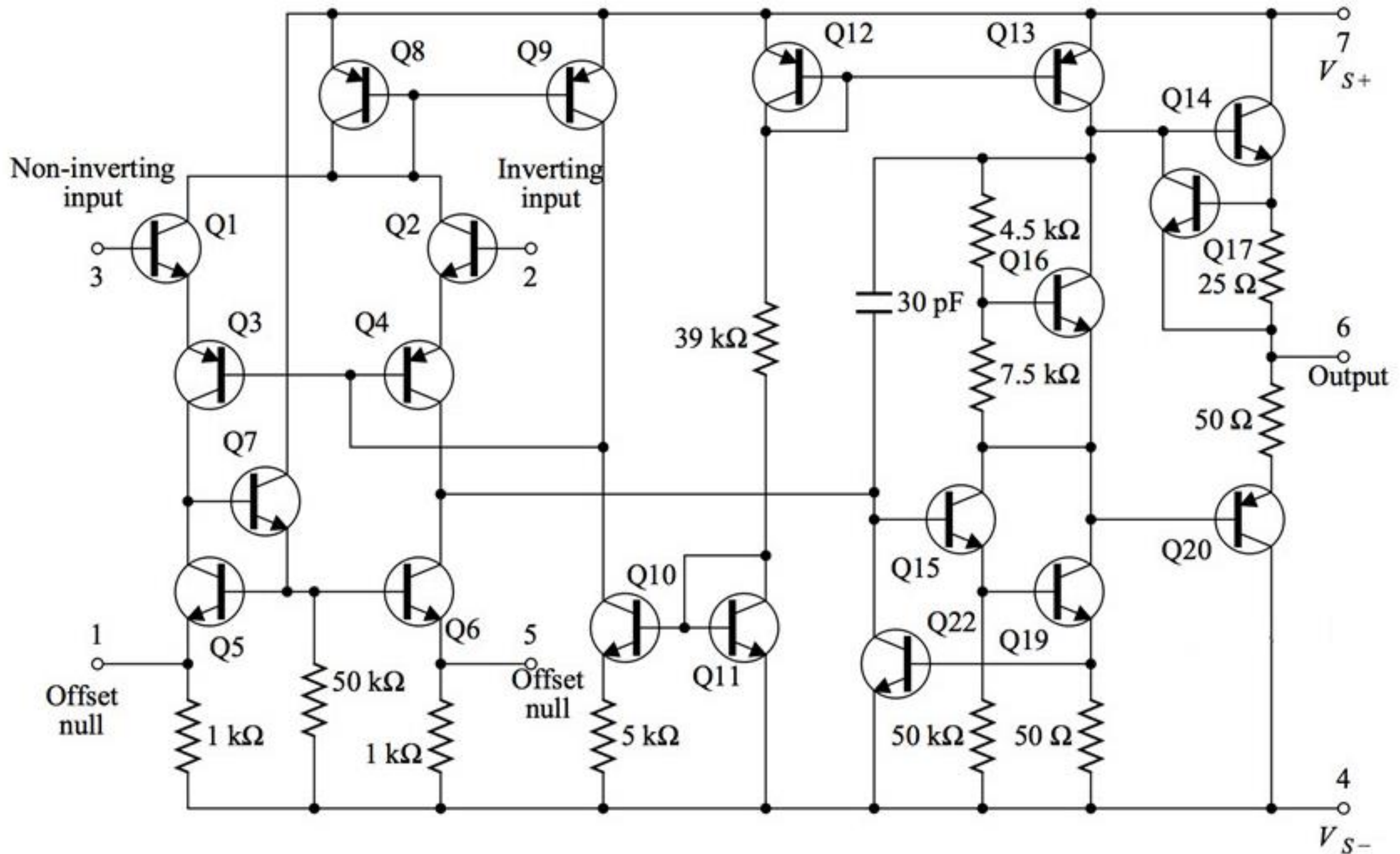The Internal Circuit of a Typical Operational Amplifier




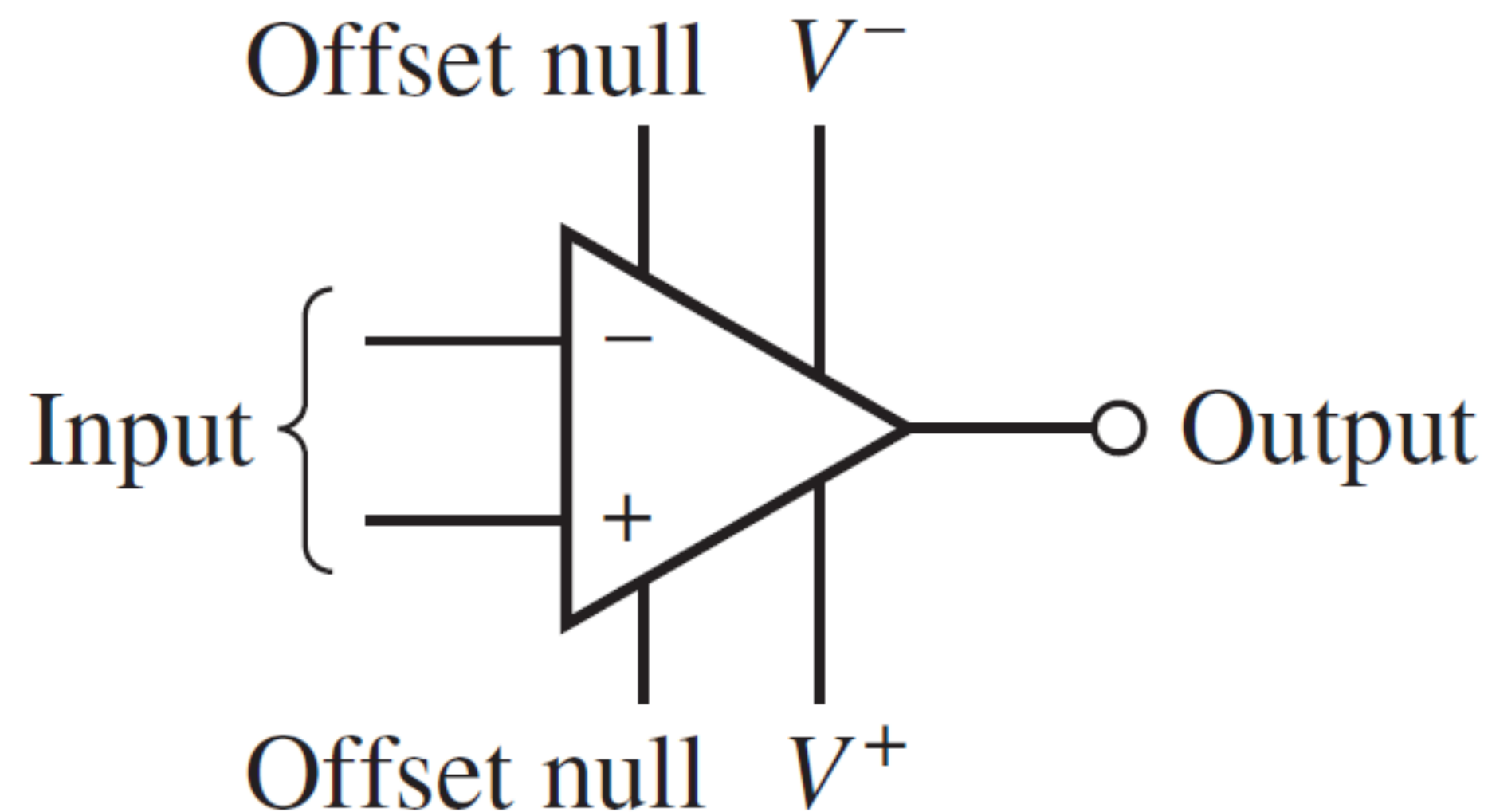- An operational amplifier (Op-Amp) is generally represented by the following symbol and includes the following pins:
- **Input Pins:** *Input*
- **Output Pin:** *Output*
- **Power Supply Pins:** V^+ , V^-
- **Offset Adjustment Pins:** *Offset*



Op-Amp Symbol

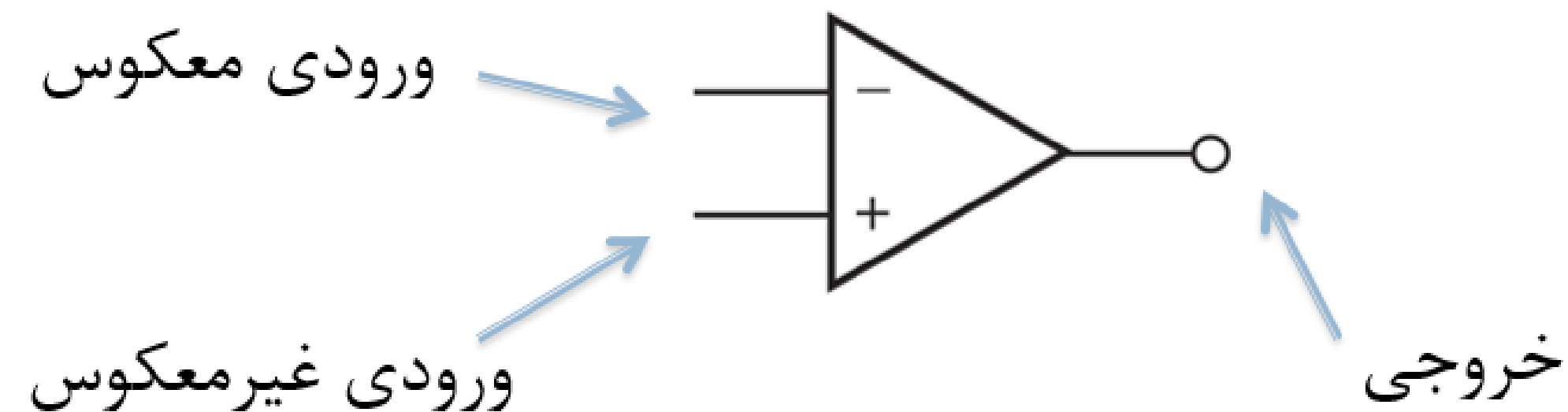- ✓ Let us focus on the **input** and **output pins**, assuming the other pins are connected to appropriate voltage levels.
- ✓ An operational amplifier functions as a **differential amplifier**, meaning it amplifies the difference between its input signals.




Precise Model of an Op-Amp

➤ A circuit that operates as a voltage amplifier can be modelled using the following equivalent circuit.

➤ This model includes:

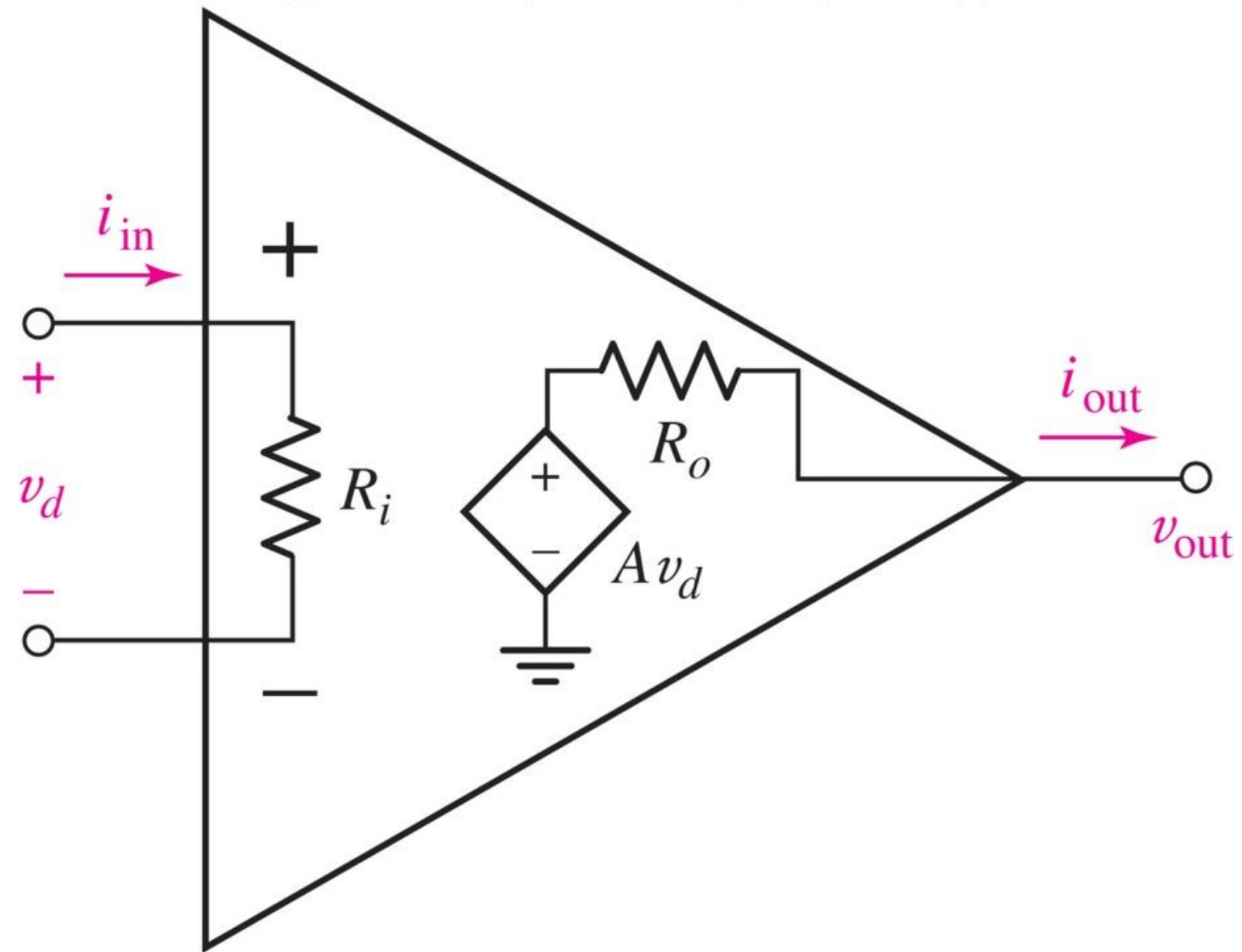
- **Input Resistance (R_i)**
- **Output Resistance (R_o)**
- **Open-Loop Gain (A)**



✓ In the circuit below, what is the gain of the amplifier?

➤ $KCL_1: \frac{-v_d - v_{in}}{R_1} + \frac{-v_d - v_{out}}{R_f} + \frac{-v_d}{R_i} = 0$

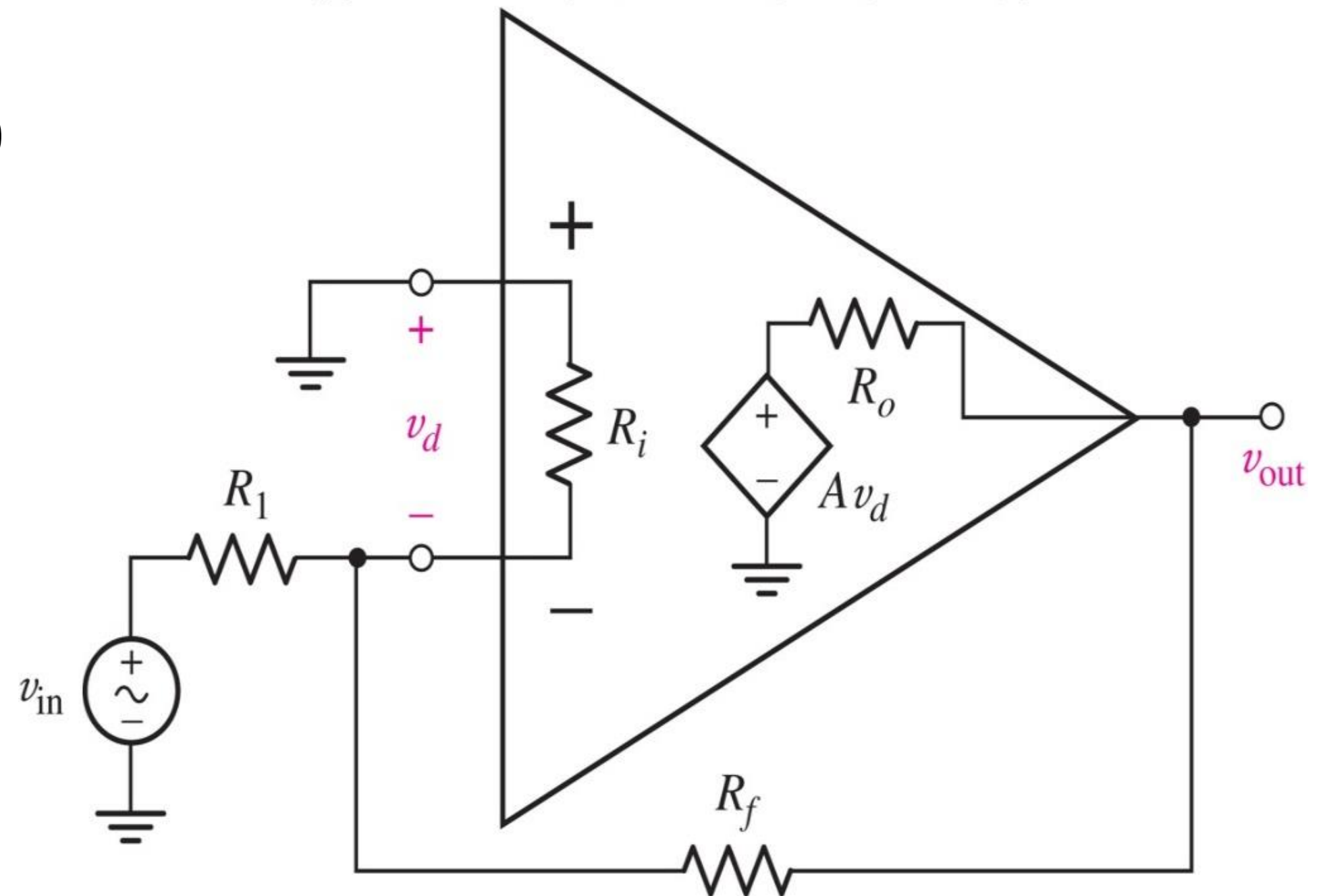➤ $KCL_2: \frac{v_{out} + v_d}{R_f} + \frac{v_{out} - Av_d}{R_o} = 0$



✓ By solving the system of equations and eliminating v_d , we obtain:

$$\blacktriangleright A_v = \frac{v_{out}}{v_i} = \left[\frac{R_o + R_f}{R_o - A R_f} \left(1 + \frac{R_1}{R_f} + \frac{R_1}{R_i} \right) - \frac{R_1}{R_f} \right]^{-1}$$

➤ Example Solution for the Inverting Amplifier Using LM741 Specifications


➤ $A = 200000$

➤ $R_i = 2M\Omega$

➤ $R_o = 75\Omega$

➤ If $R_f = 47$ and $R_1 = 4.7$

➤ Then: $A_v = -9.999$

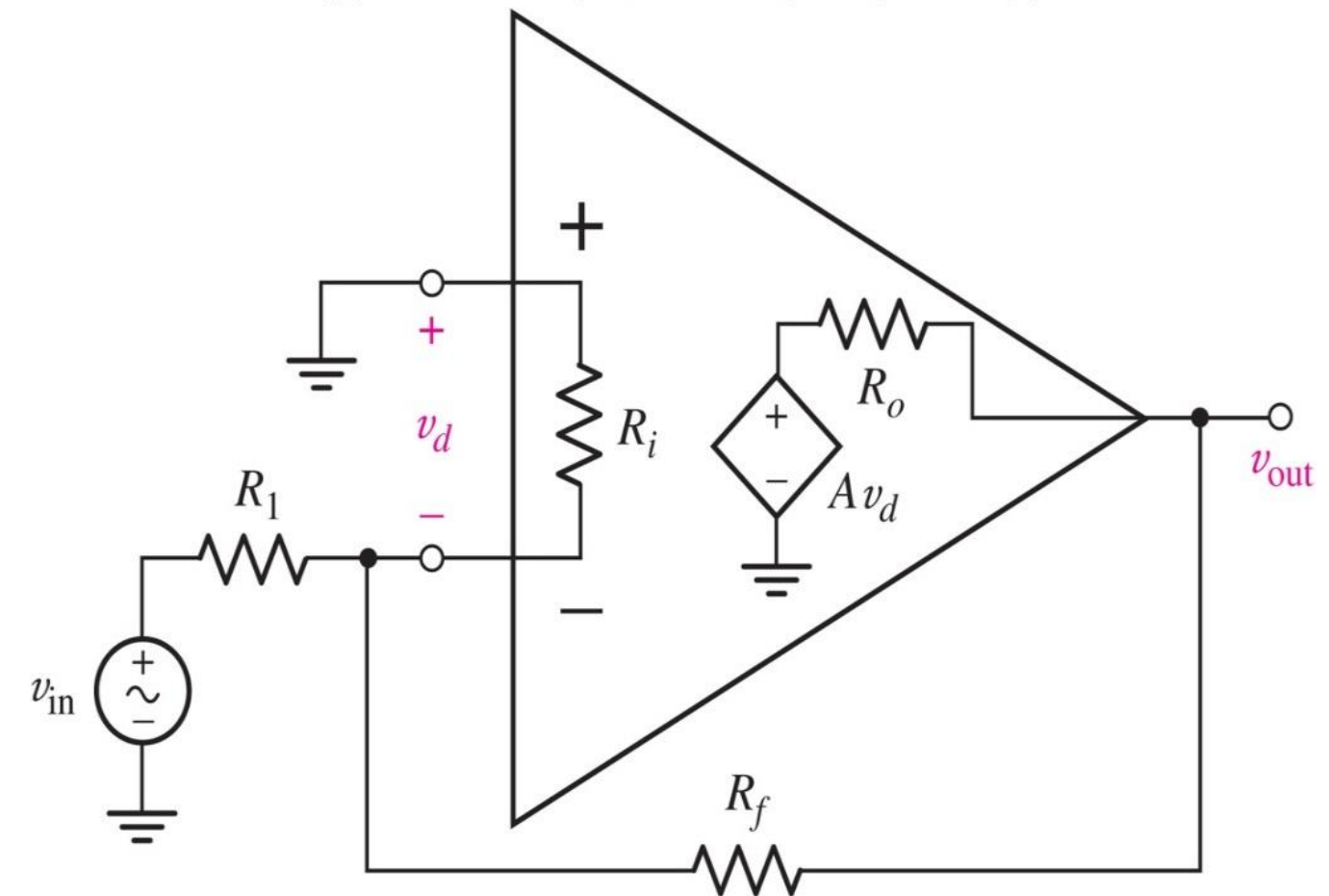

- ✓ **High Input Resistance:**(in the range of mega-ohms to tera-ohms)
 - To ensure that the maximum voltage of the source is applied across its input.
- ✓ **Low Output Resistance:**(in the range of a few ohms to a few tens of ohms)
 - to ensure that the entire output voltage of the amplifier is delivered to the load.
- ✓ **Adjustable Gain:**(achieved by applying feedback resistance):
 - As observed in the circuit shown, provided that A is sufficiently large, the gain of the amplifier can be approximated with high accuracy as $A_v \approx -\frac{R_f}{R_1}$.


Ideal Model

➤ In the ideal case, when $A = \infty$, $R_i = \infty$, and $R_o = 0$, the behaviour of the operational amplifier can be described as follows:

➤ Since v_{out} has a finite value (it cannot exceed the supply voltage),


$$v_d = \frac{v_{out}}{A} \approx 0.$$

➤ As a result, $i_{in} \approx 0$.

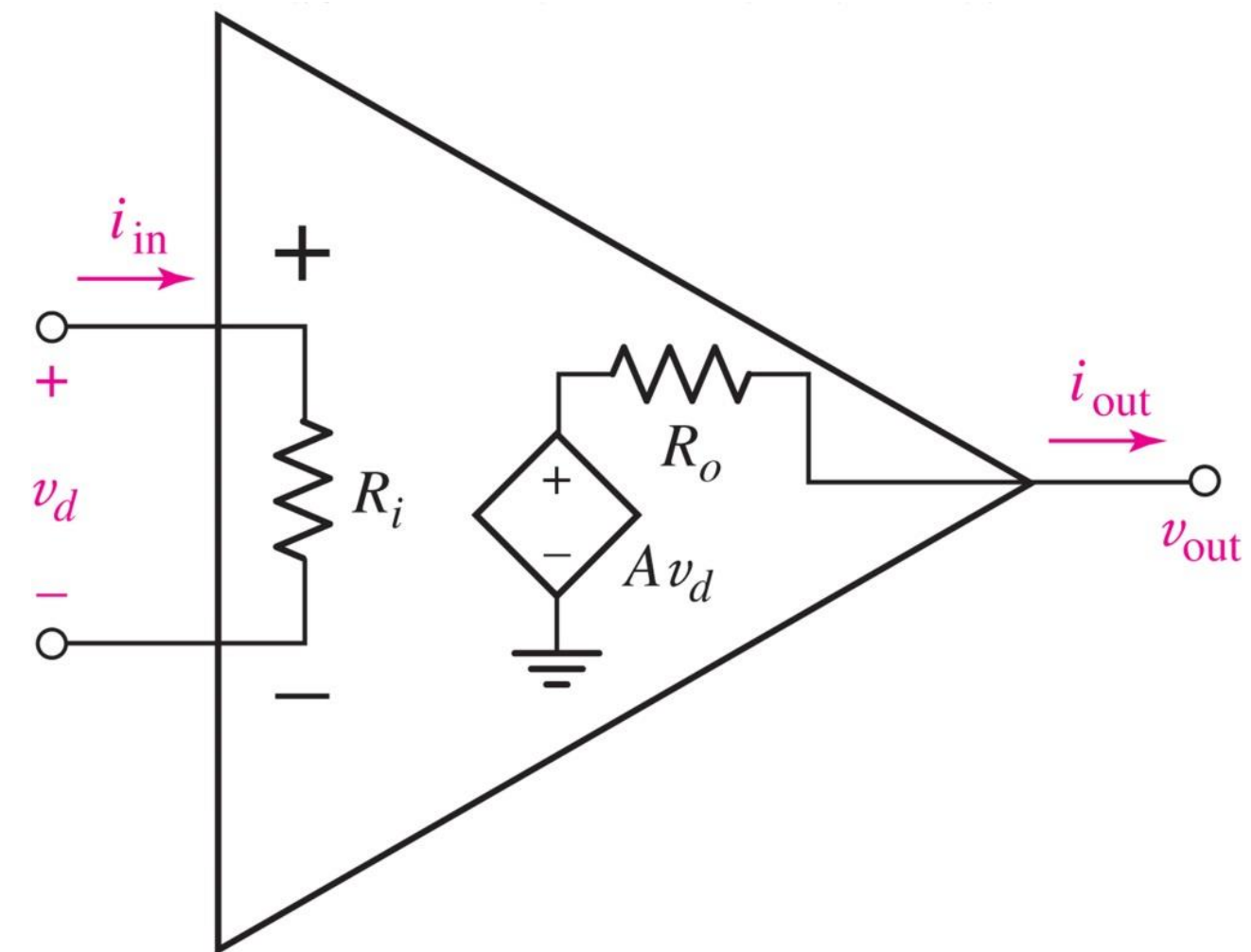


Rules of the Ideal Model:

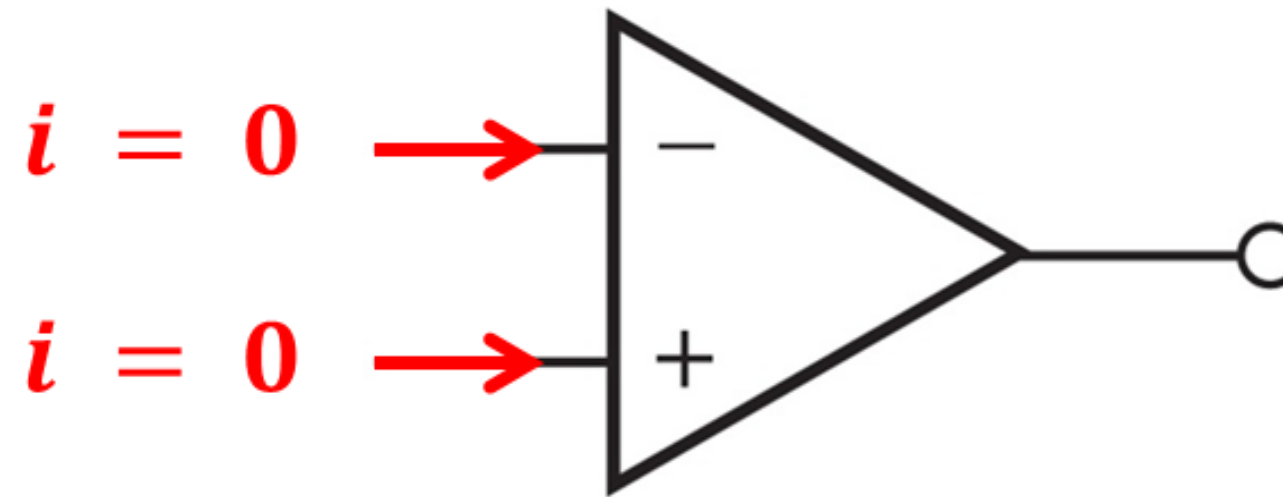1.No current flows through the input terminals.




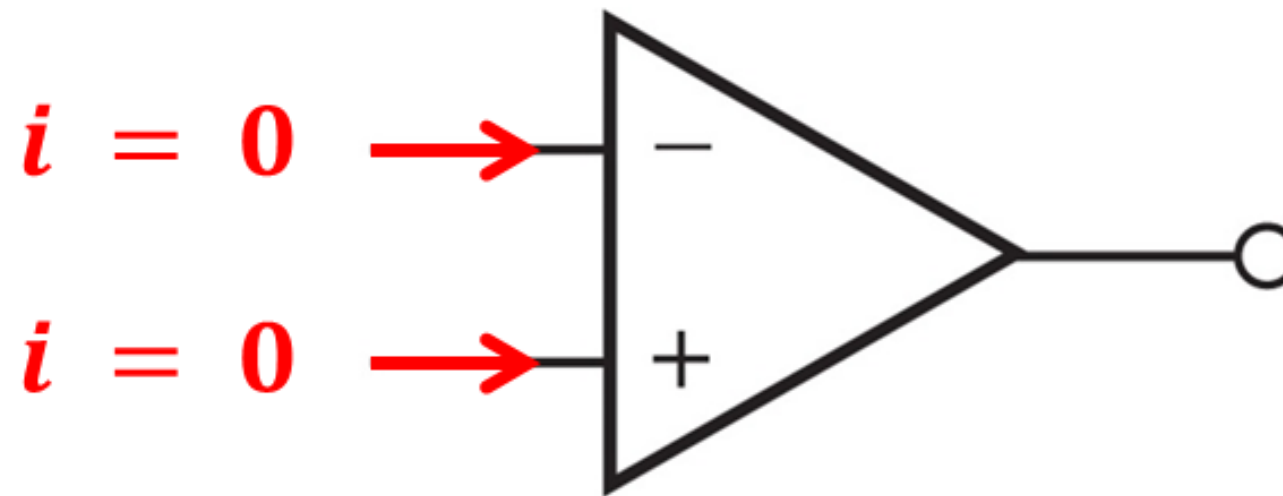2.The voltage difference between the two input terminals is zero.




Inverting Amplifier

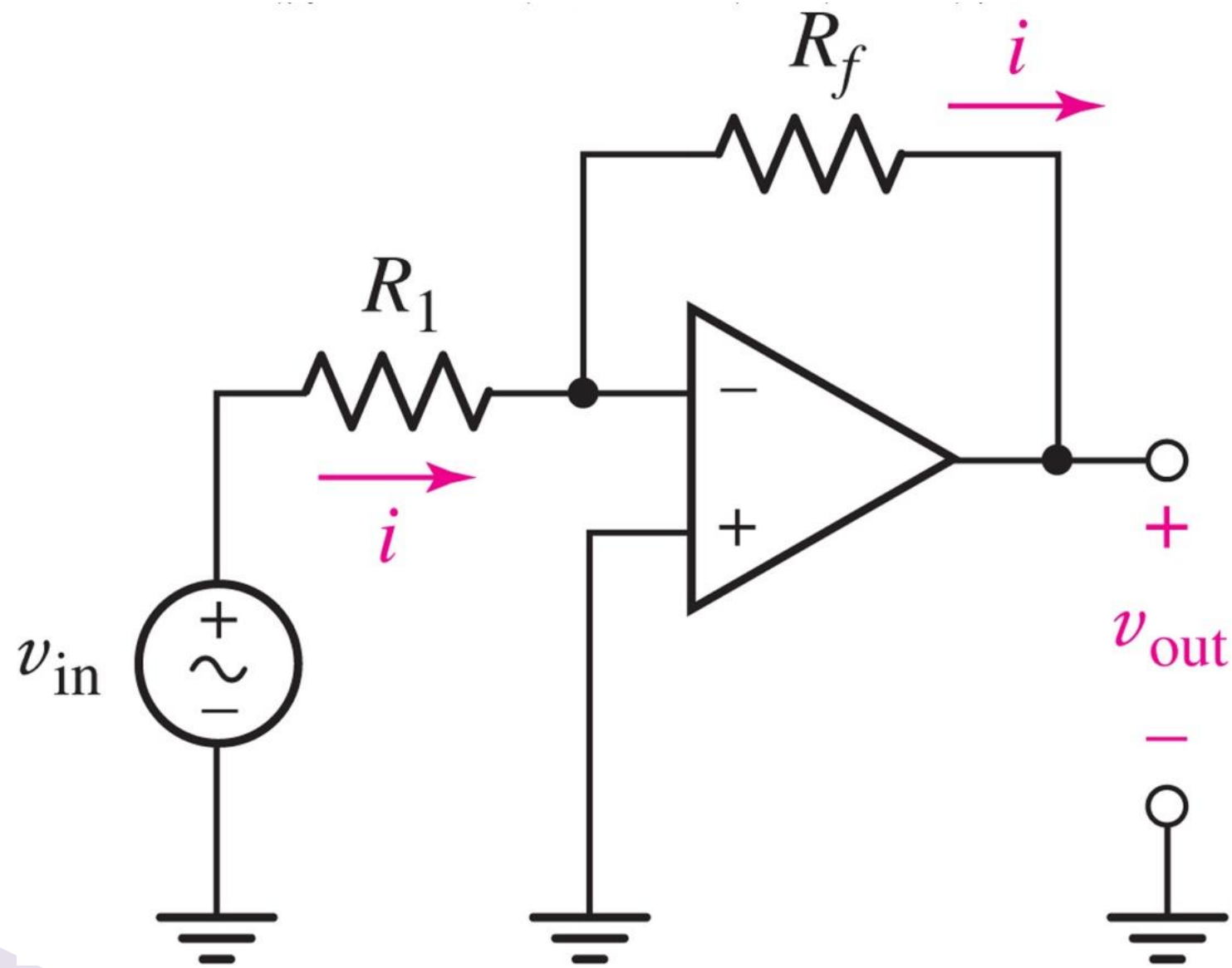- ✓ By applying KVL and using the rules of the ideal operational amplifier, we have:



$$v_{out} = -\frac{R_f}{R_1} v_{in}$$


Non-Inverting Amplifier

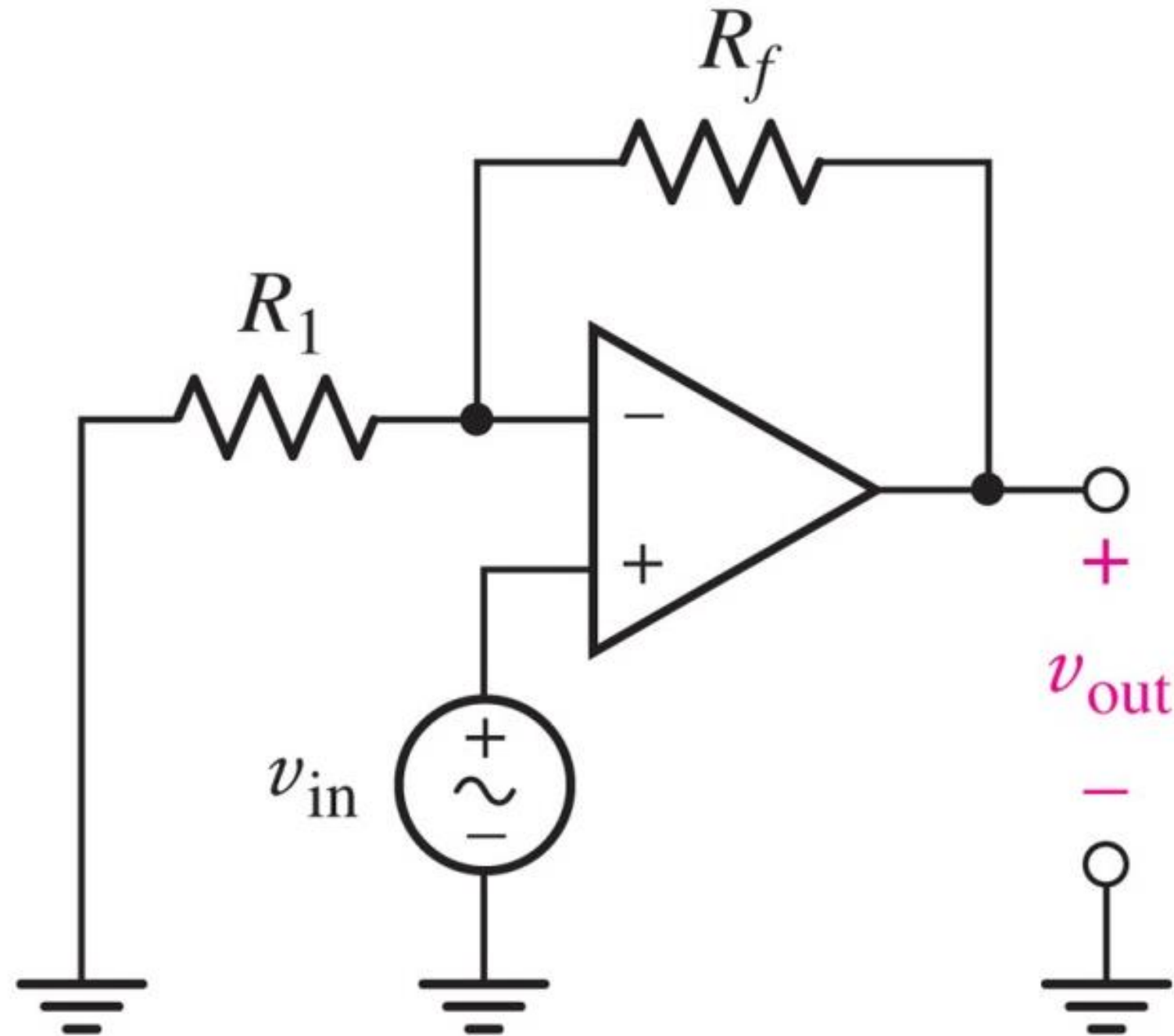


$$v_{out} = \left(1 + \frac{R_f}{R_1} \right) v_{in}$$

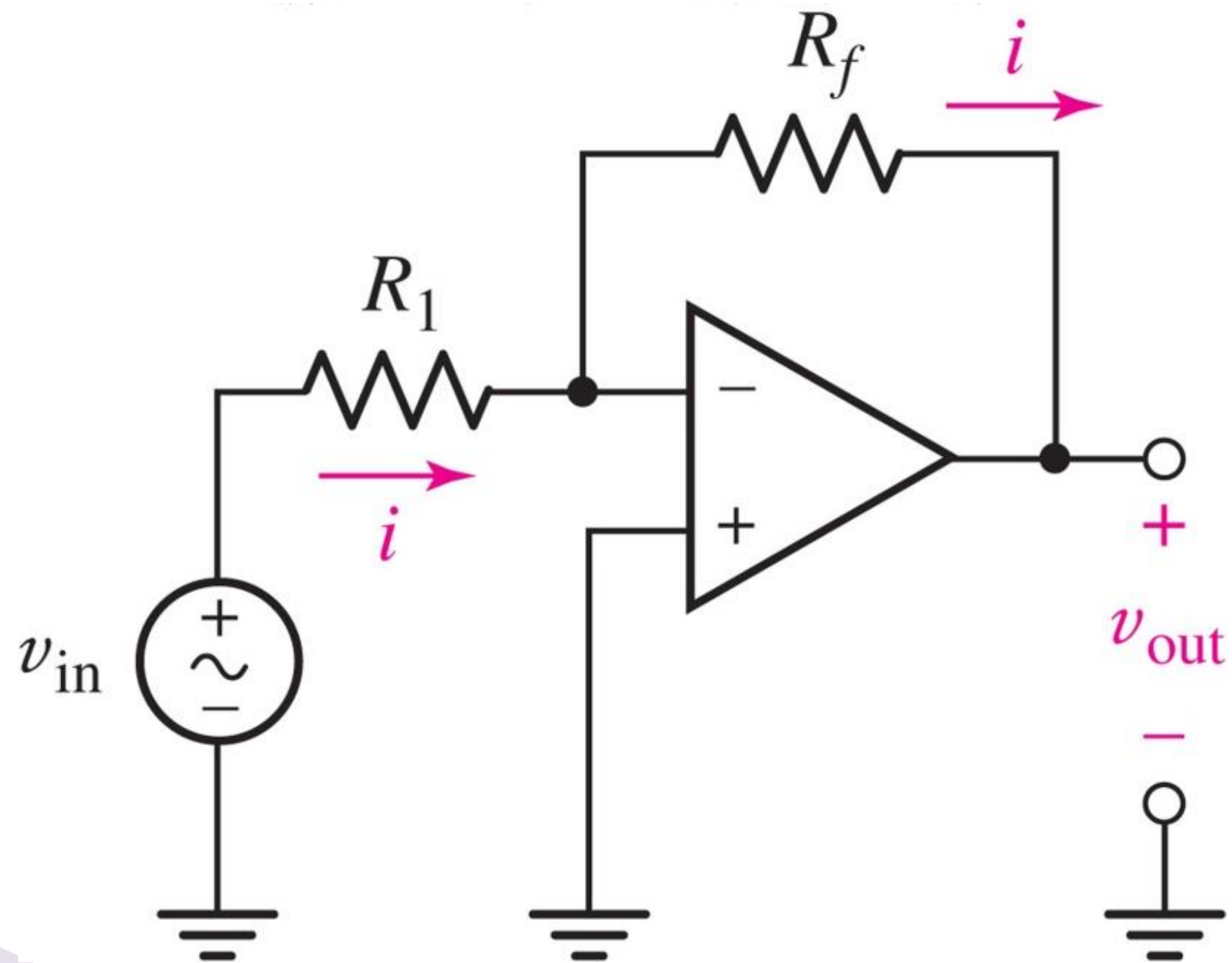Example


- $v_{in}(t) = 5\sin 3t \text{ mV}$, $R_f = 47\text{K}\Omega$, $R_1 = 4.7\text{K}\Omega$



$$v_{out}(t) = -50 \sin 3t \text{ mV}$$

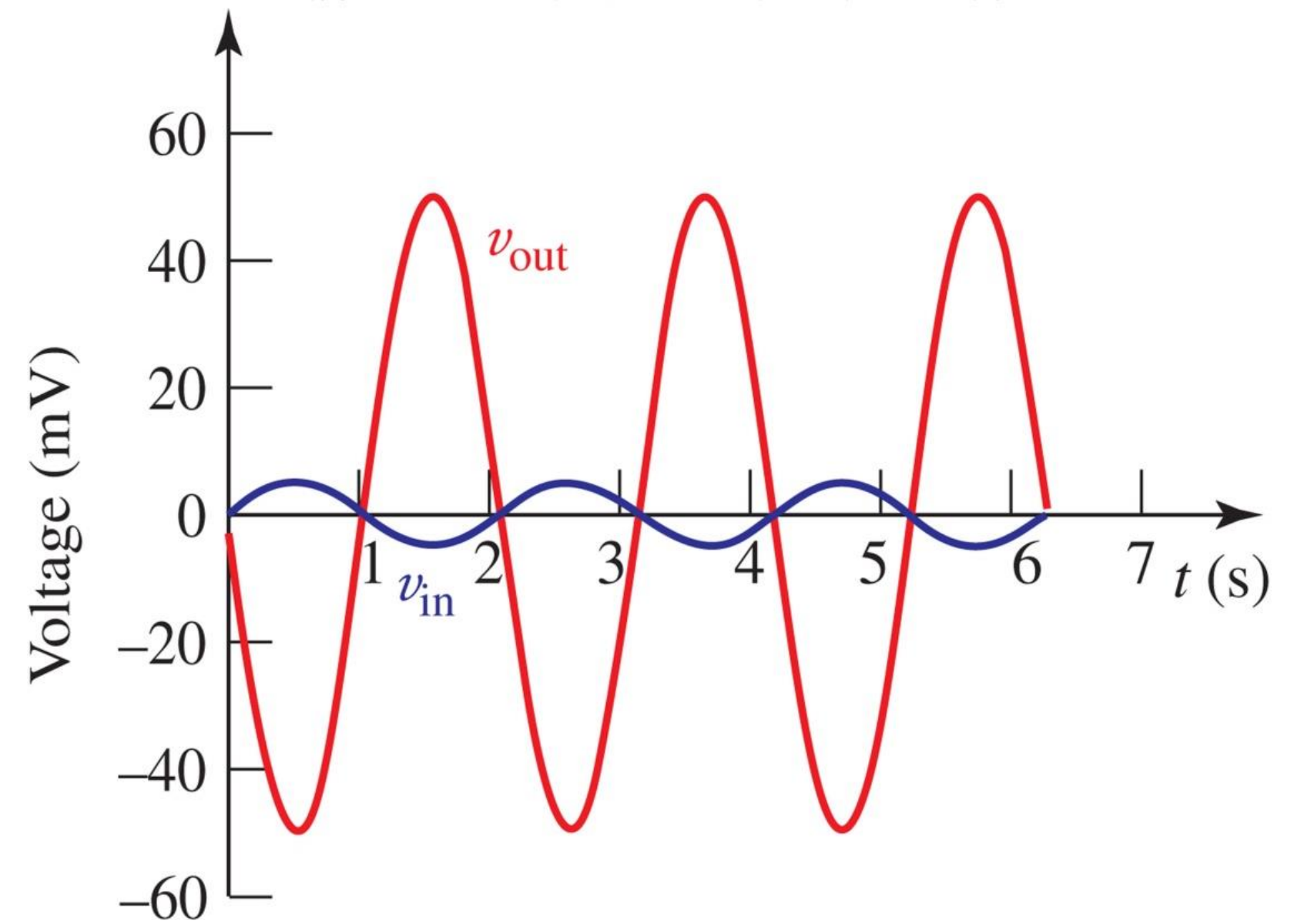


Voltage Follower (Buffer)

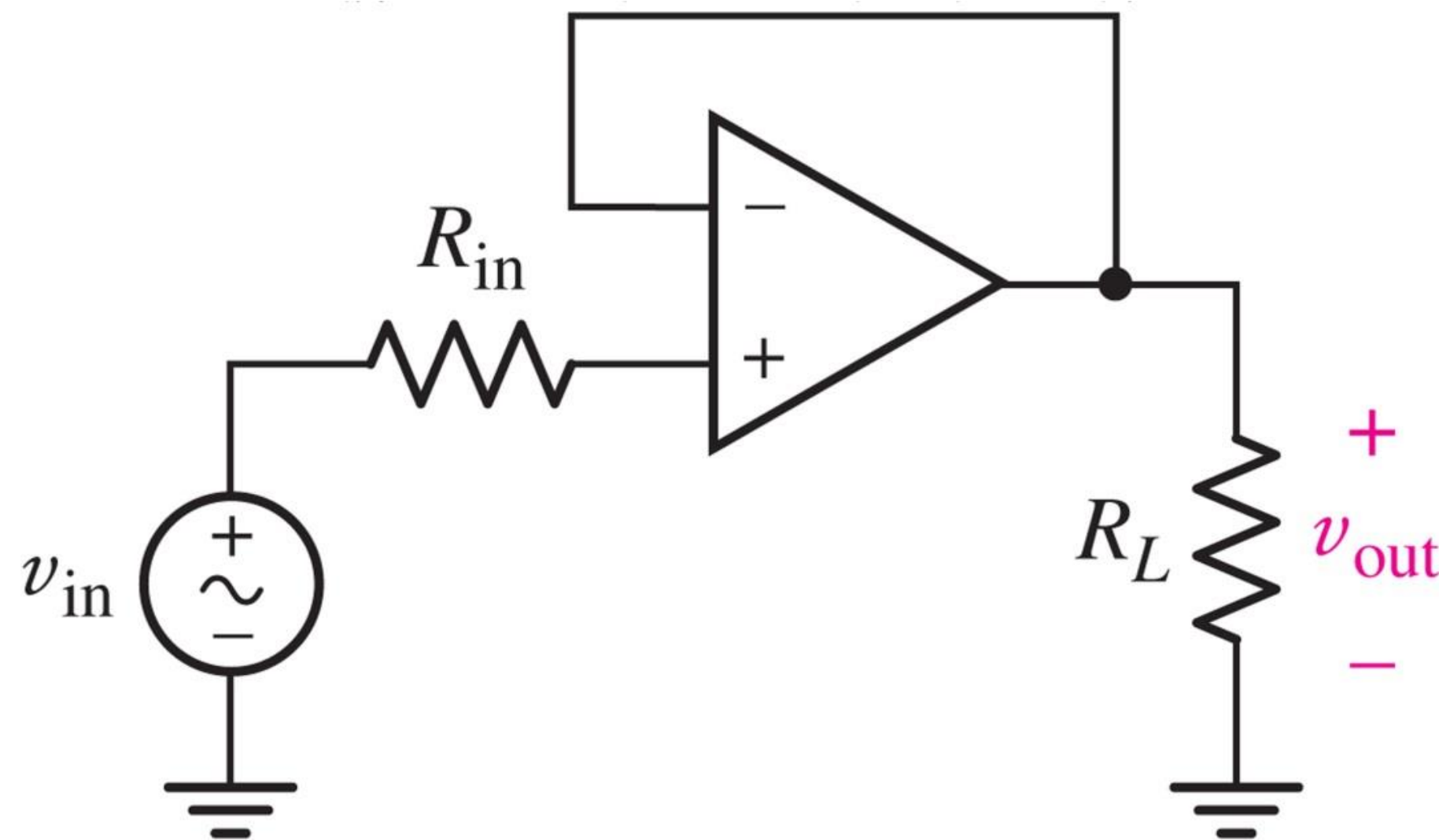

$$v_{out}(t) = v_{in}(t)$$

1. The output voltage of the buffer is independent of the load resistance (R_L). The buffer can supply the required current to maintain a constant output voltage, even if R_L changes.
2. This circuit eliminates the effect of the source's input resistance by presenting a very high input resistance to the source and a very low output resistance to the load.


Analog Summing Circuit

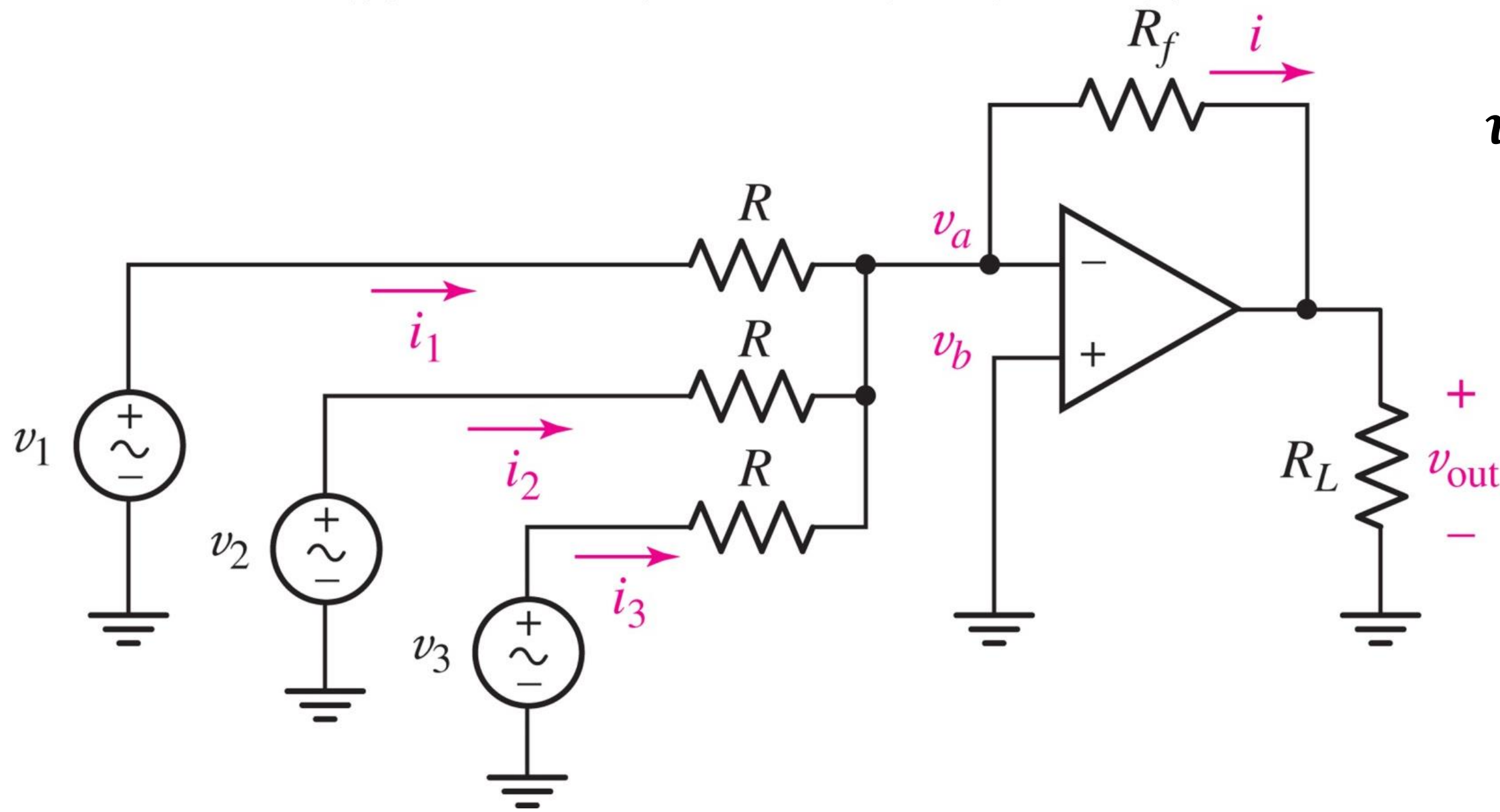

$$v_{out} = -\frac{R_f}{R_1}(v_1 + v_2 + v_3)$$

- ✓ This circuit performs the addition of input signals and amplifies the result by a factor of $-\frac{R_f}{R_1}$.

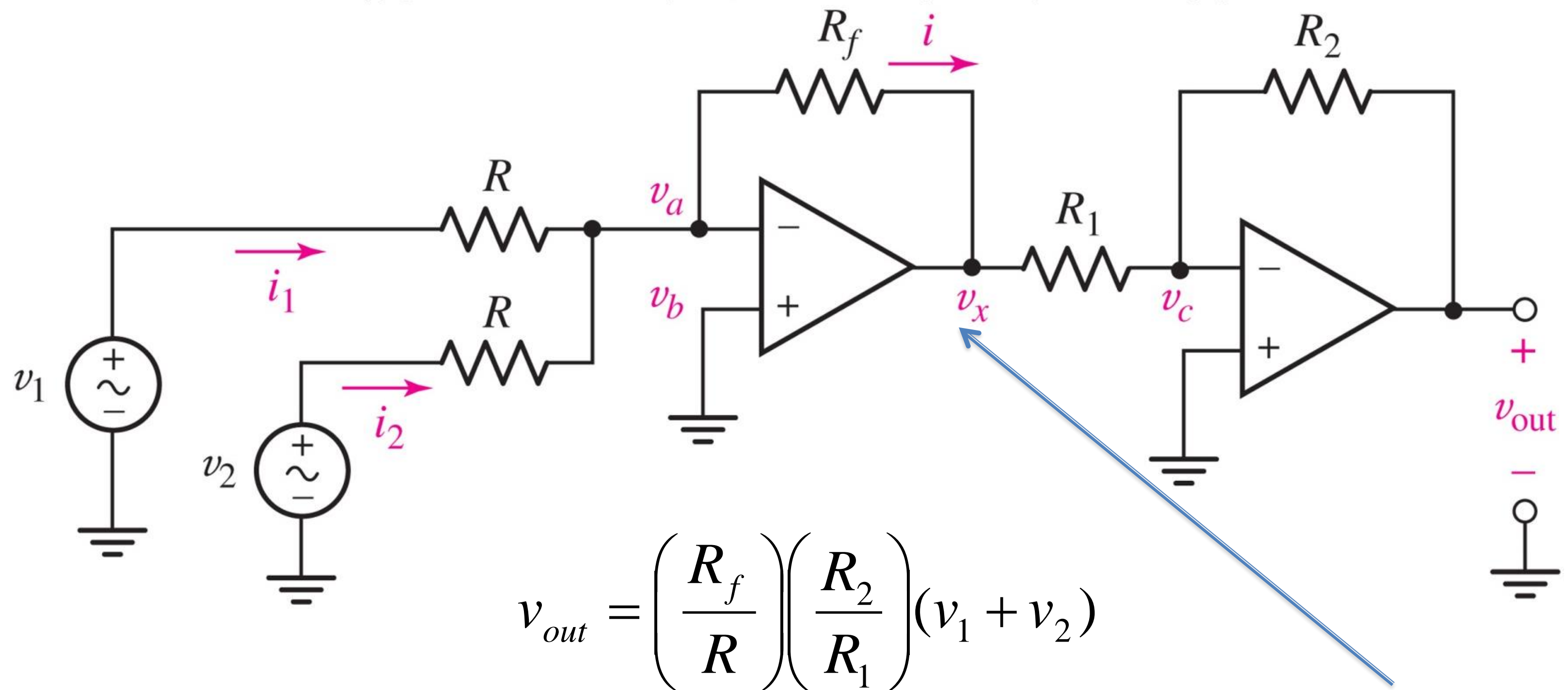
Cascading Multiple Operational Amplifiers



- ✓ The output voltage of each stage is independent of the subsequent stage. (**Why?**)
- ✓ As a result, **Op-Amp** can be cascaded without any alteration in their individual gains.


Op-Amp as an Ideal Voltage Source
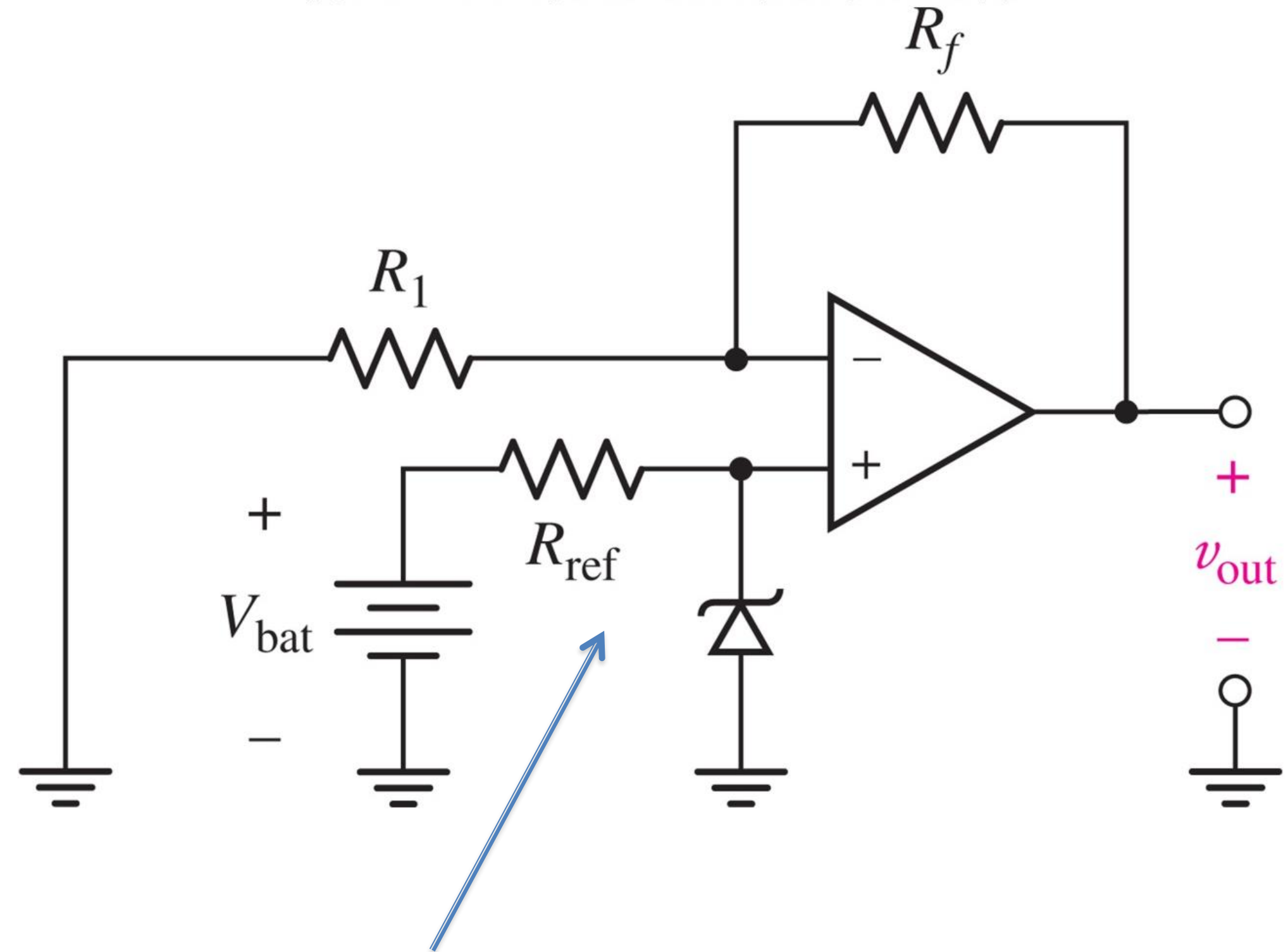
$$v_{out} = \left(1 + \frac{R_f}{R_1}\right) V_Z$$



This circuit resembles the voltage regulator using a Zener diode, which we have encountered before.

Op-Amp as an Ideal Current Source

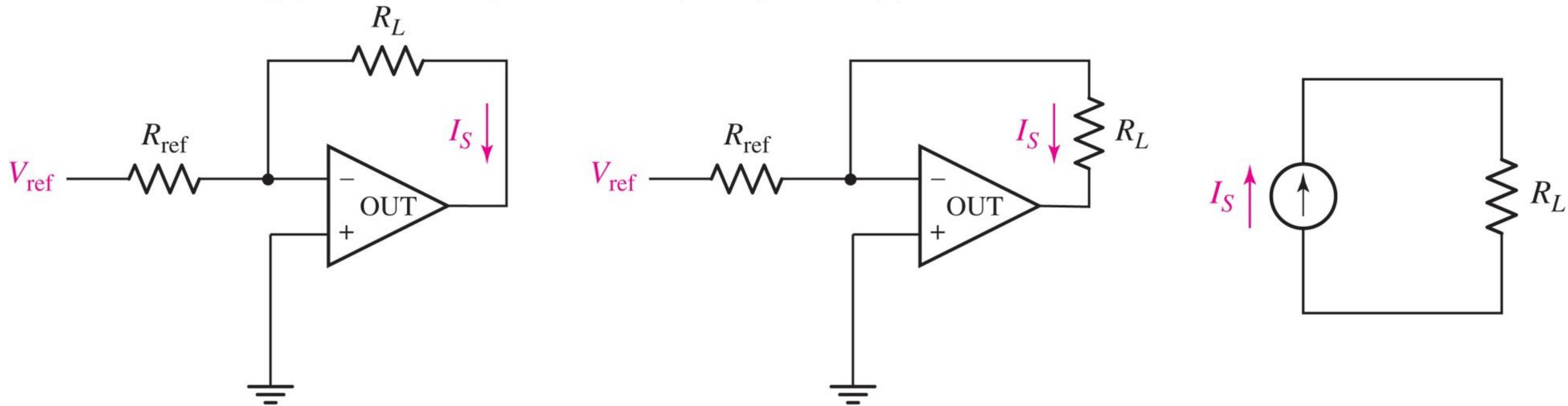


- Using a reference voltage V_{ref} and a resistor R_{ref} , an ideal current source can be constructed with a current:

$$I_S = \frac{V_{ref}}{R_{ref}}$$

- This current is independent of the load resistance R_L ,


Power Supplies for Op-Amp

- An operational amplifier requires power to function and perform amplification. Therefore, it must be connected to a power supply.
- Typically, equal and opposite voltage values are applied to the V^+ and V^- terminals. These voltage levels usually range between $\pm 5V$ and $\pm 24V$.
- The ground of the power supplies must be connected to the input and output ground reference of the circuit to ensure proper operation and signal integrity.

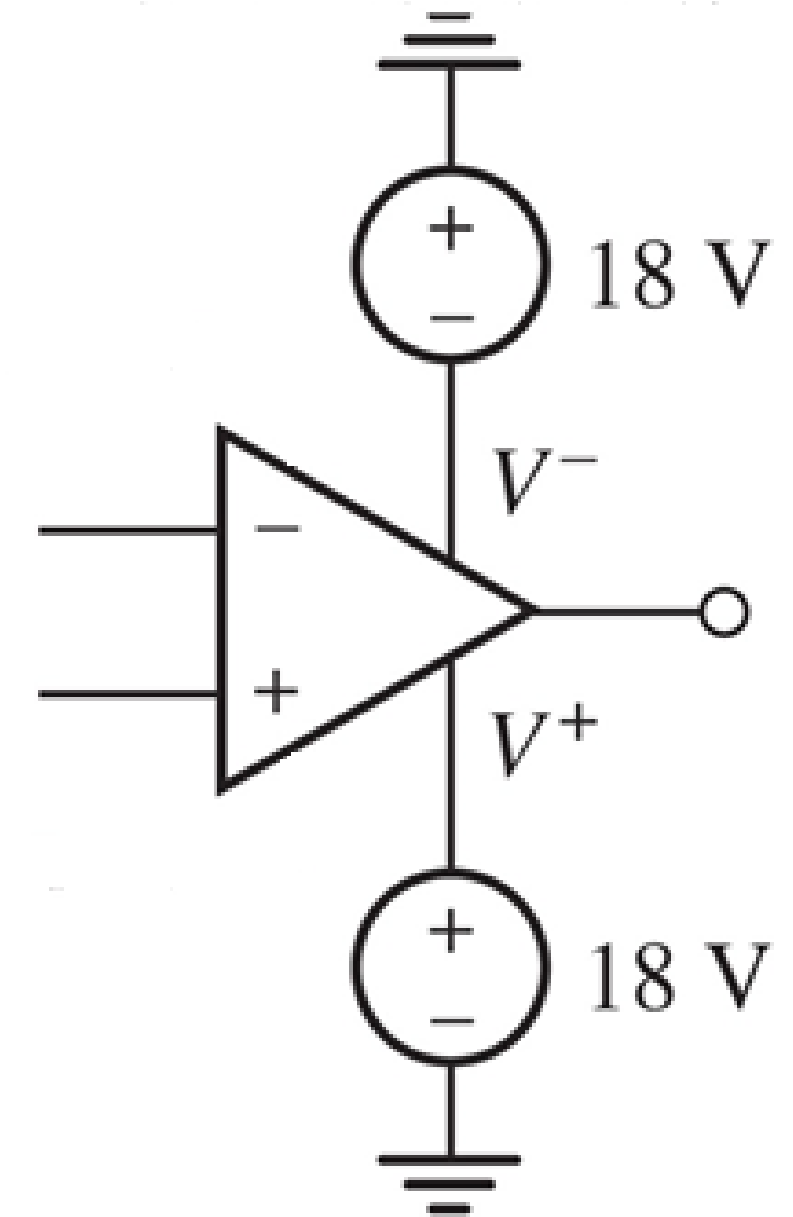

Output Saturation

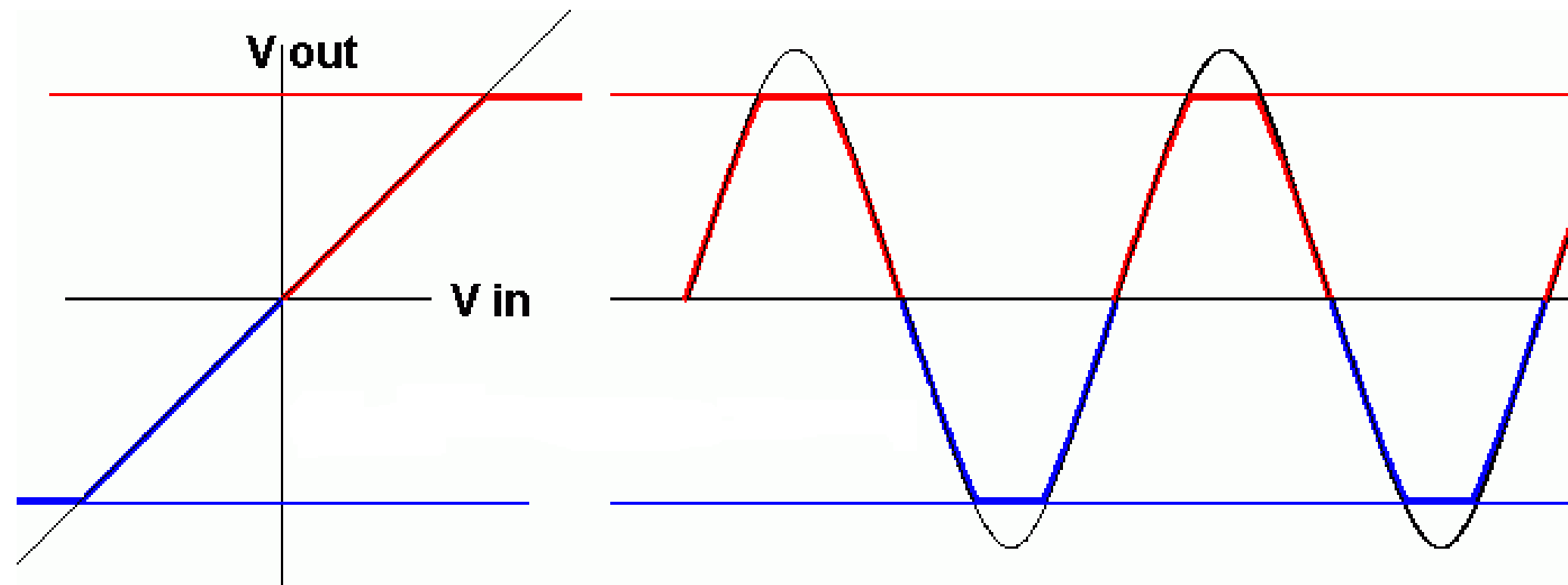- ✓ If the input signal is such that the amplified output exceeds V^+ or falls below V^- , the output will saturate.
- ✓ In this state, the output voltage remains clamped at V^+ or V^- , depending on the direction of the input signal.



The output signal enters saturation and becomes clipped


Role of Negative Feedback

- The role of negative feedback is to transform a large and undefined gain into a fixed, controlled gain.

- Why Don't We Apply Feedback to the Positive Terminal?

$$v_+ \uparrow \rightarrow v_d \uparrow \xrightarrow{v_{out} = Av_d} v_{out} \uparrow \rightarrow v_- \uparrow \rightarrow v_d \downarrow \dots$$


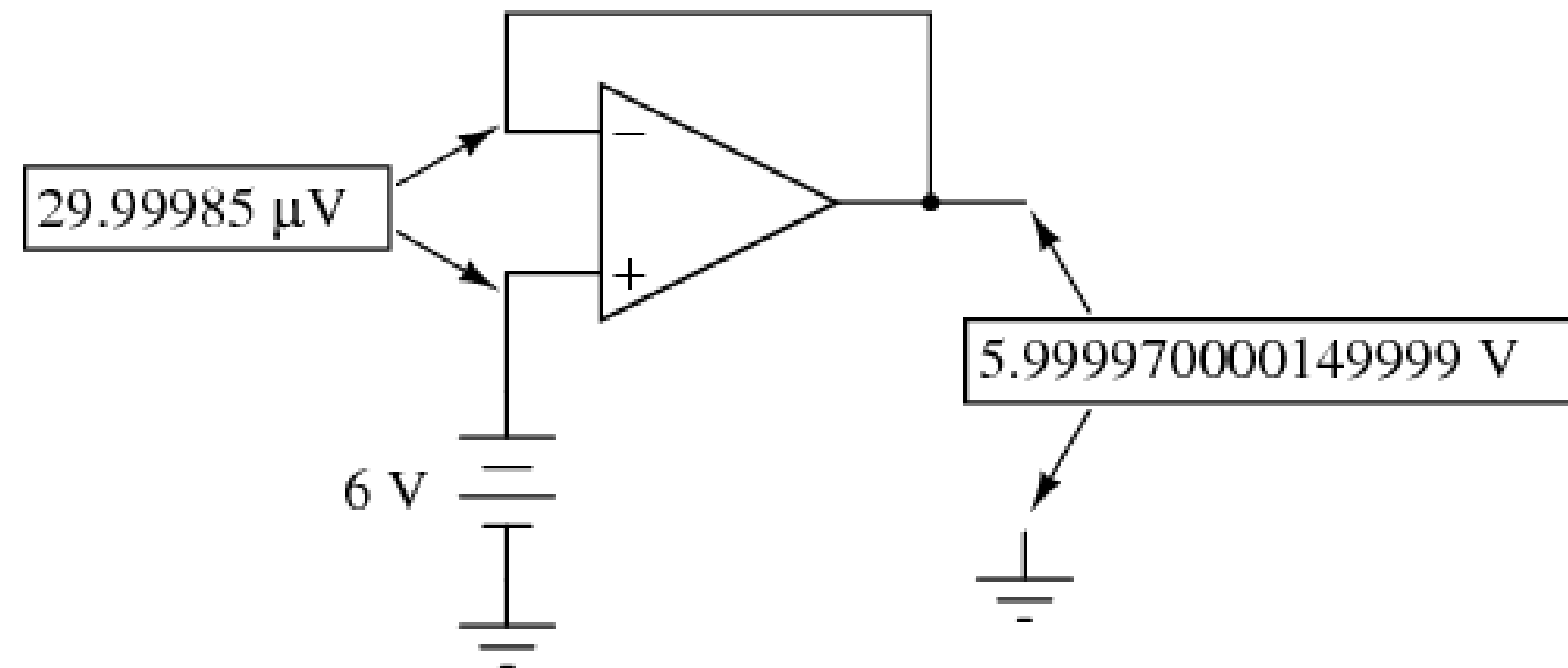
- Thus, the negative feedback stabilizes the operation by keeping v_d close to zero



Voltage Comparator


- An operational amplifier can be used as a voltage comparator when operated in open-loop configuration (without feedback).
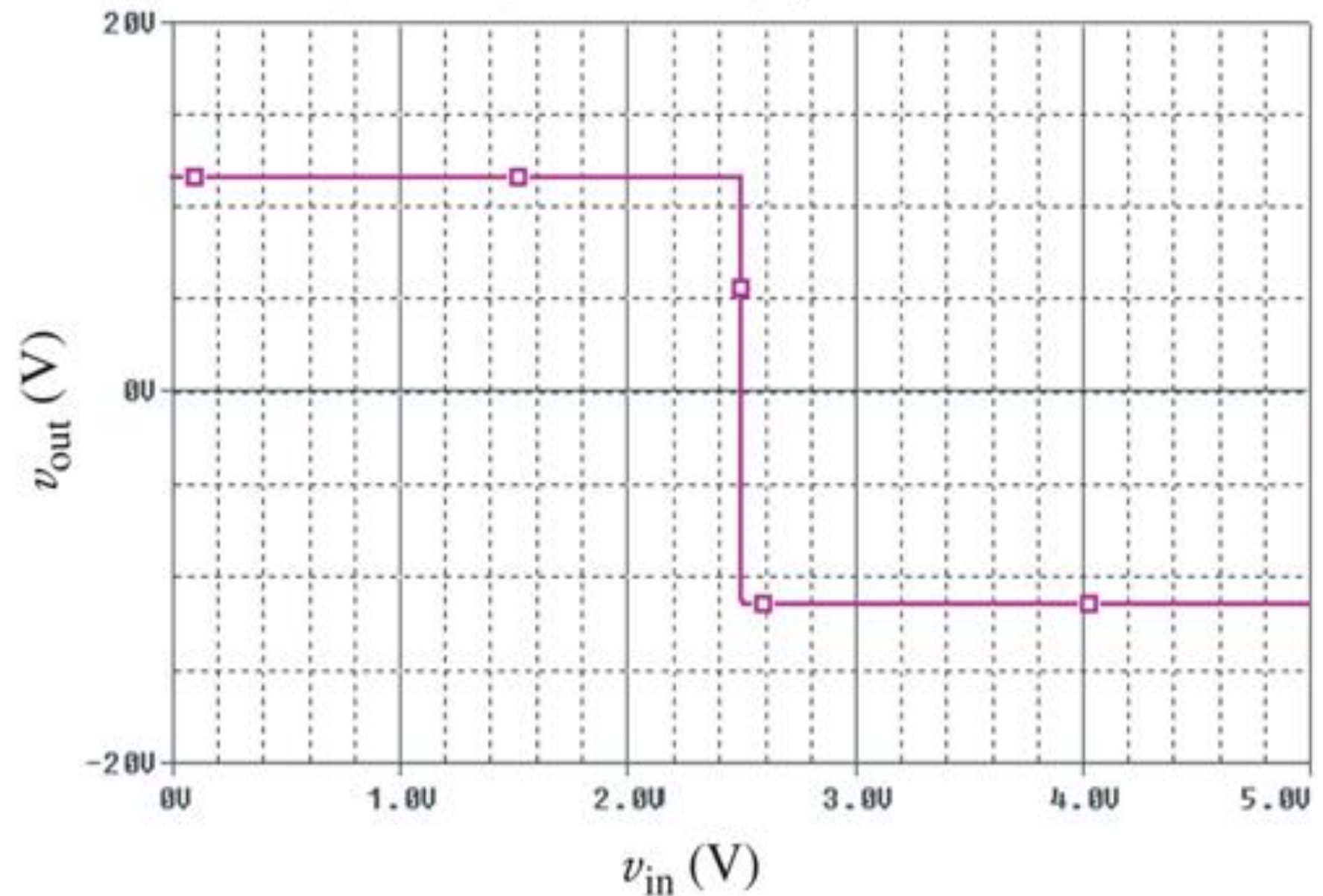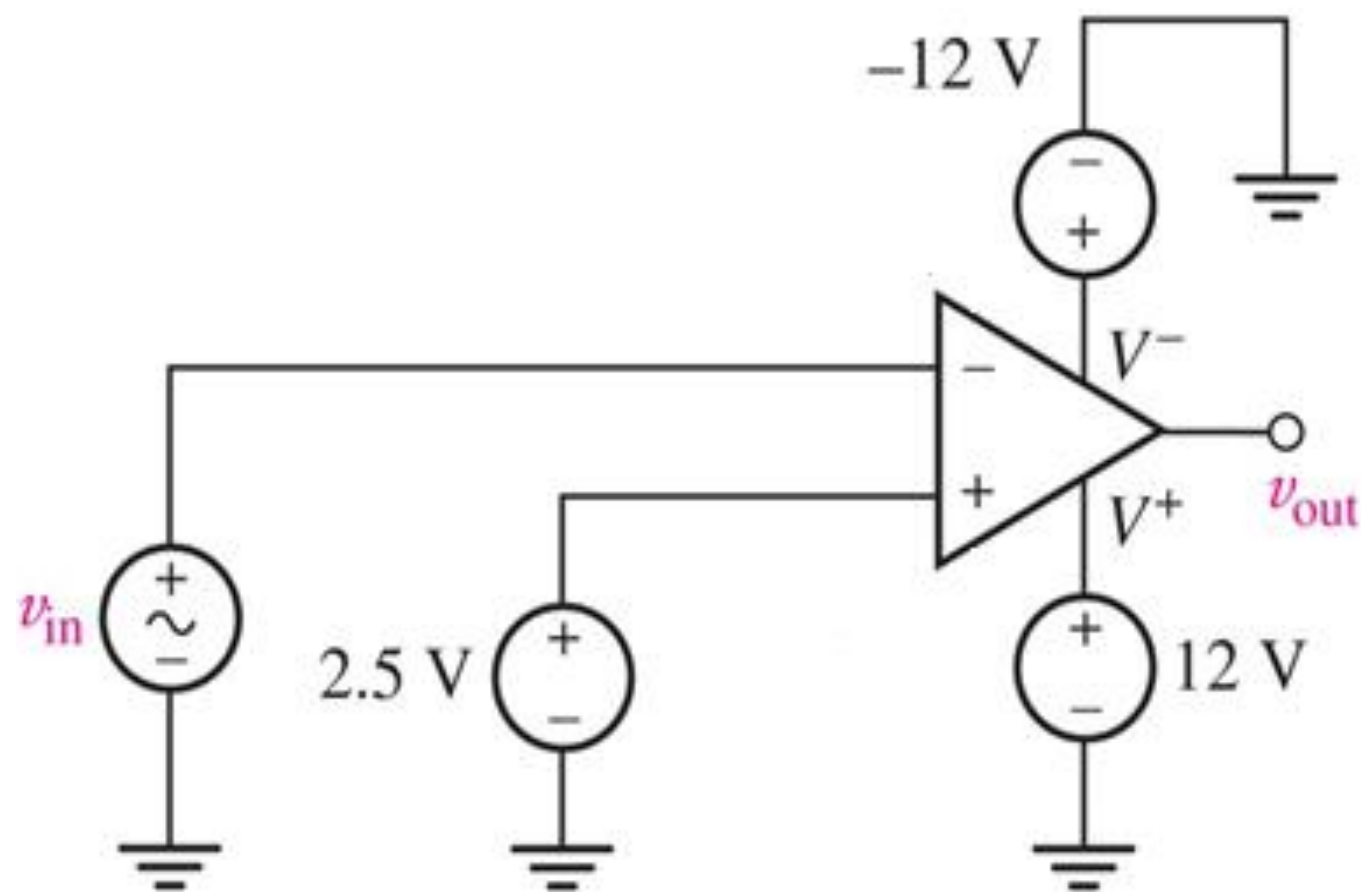
$$v_{out} = \begin{cases} 12 & v_{in} < 2.5 \\ -12 & v_{in} > 2.5 \end{cases}$$





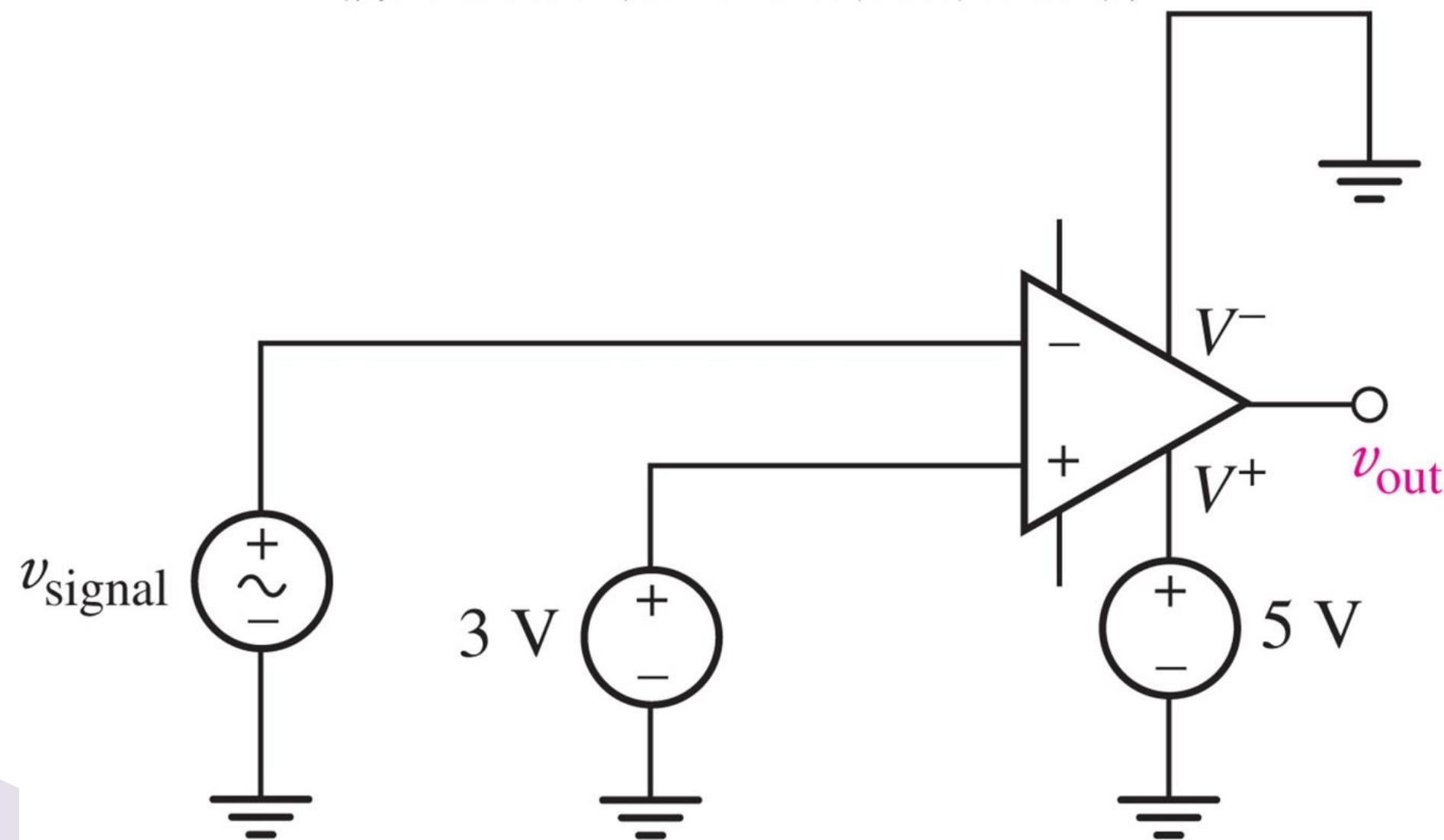Example



Assume we have a temperature sensor that generates a voltage ranging from 0 to 5 volts for temperatures between 0 and 100 degrees Celsius. Design a circuit that provides a logical output of 1 when the temperature is below 60 degrees.



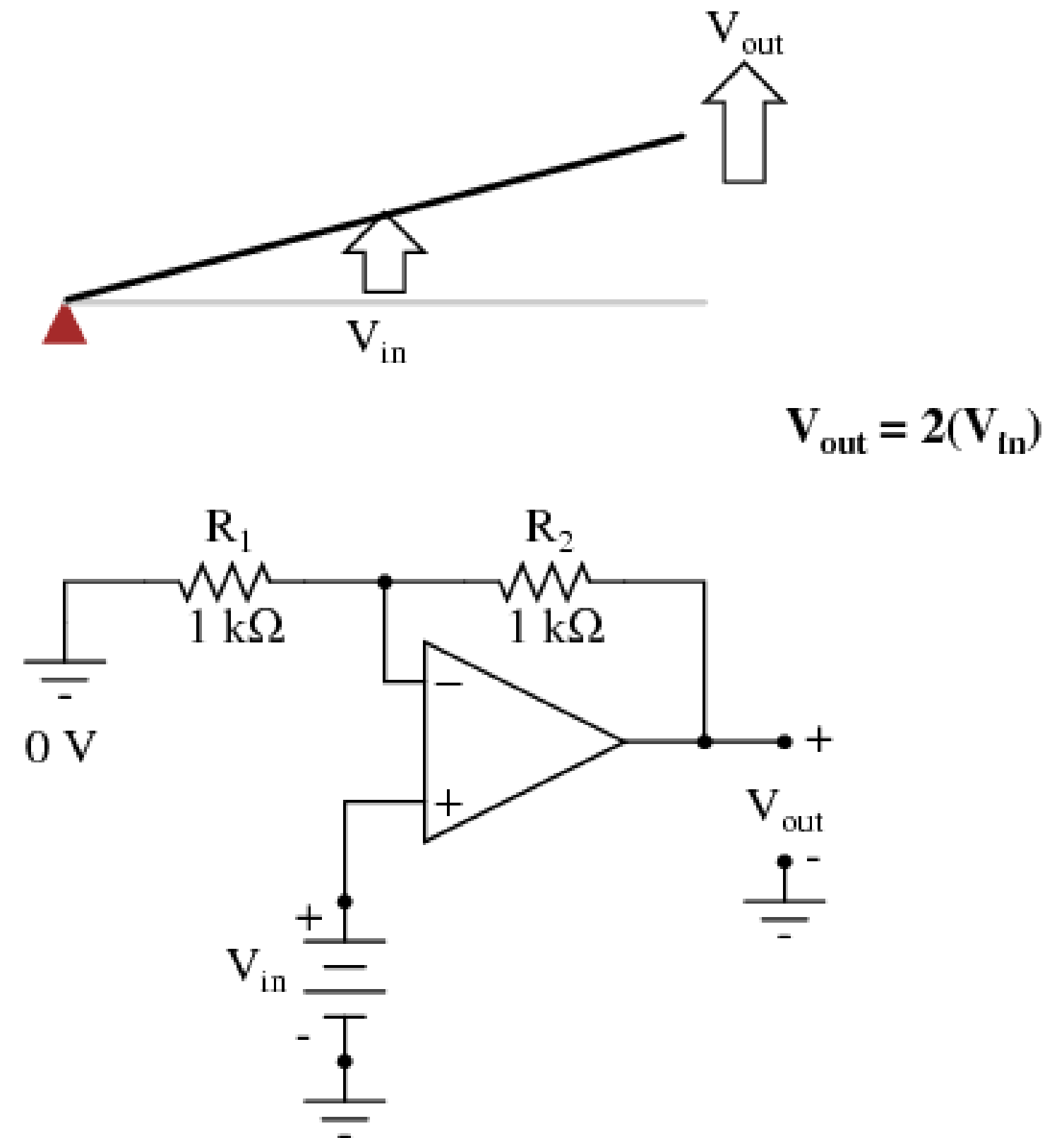
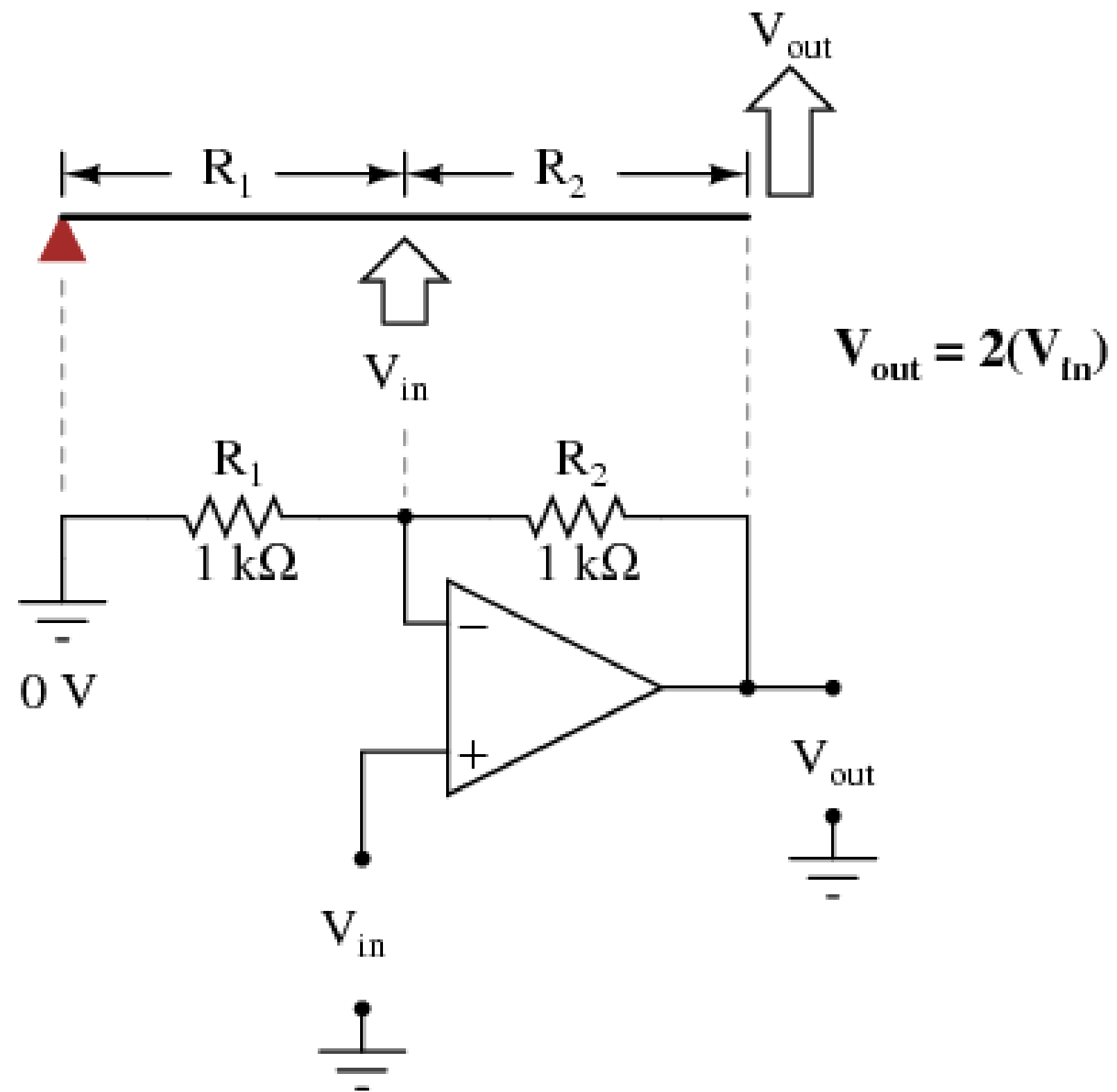
Similarity of Non-Inverting Amplifier to a Lever



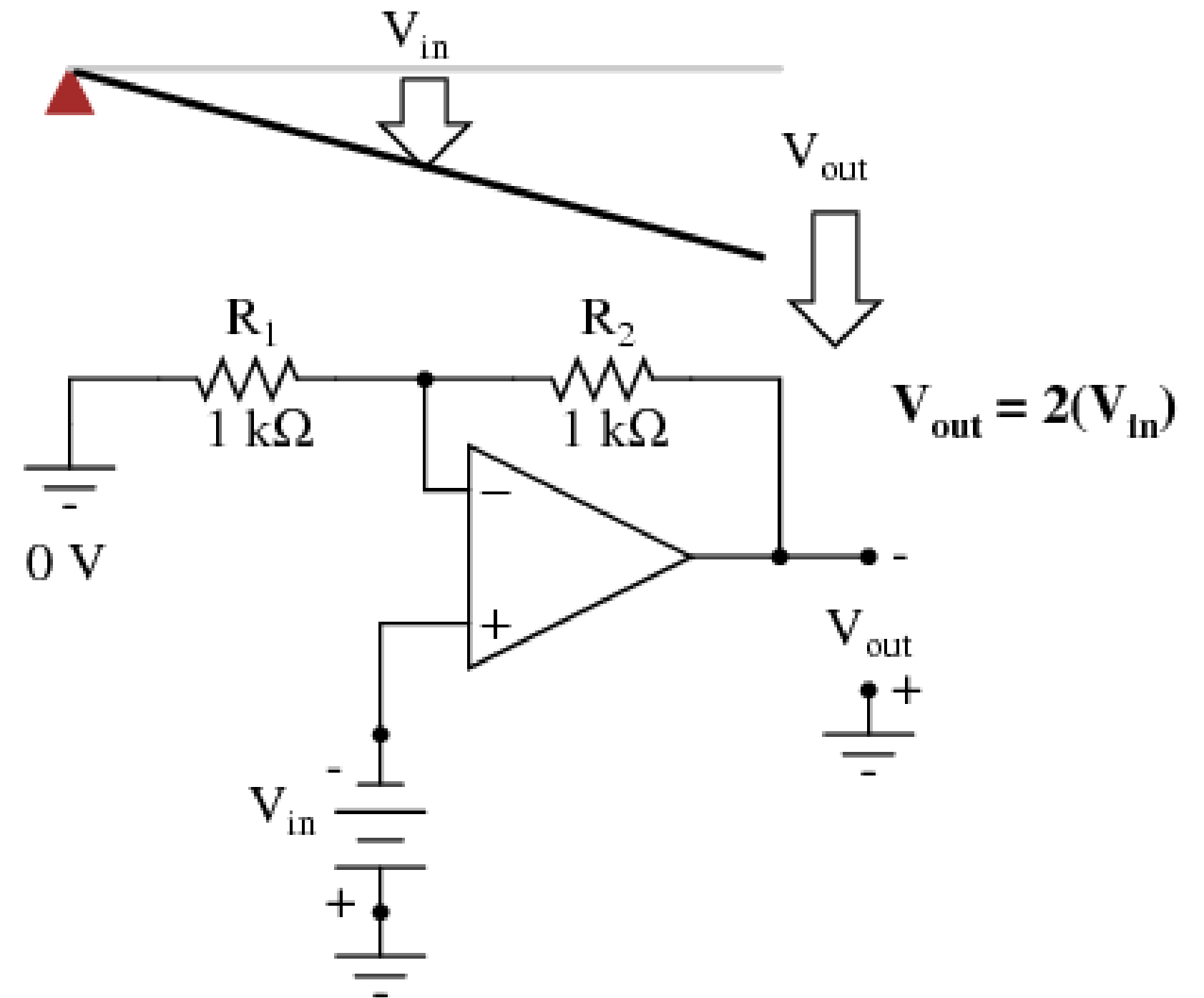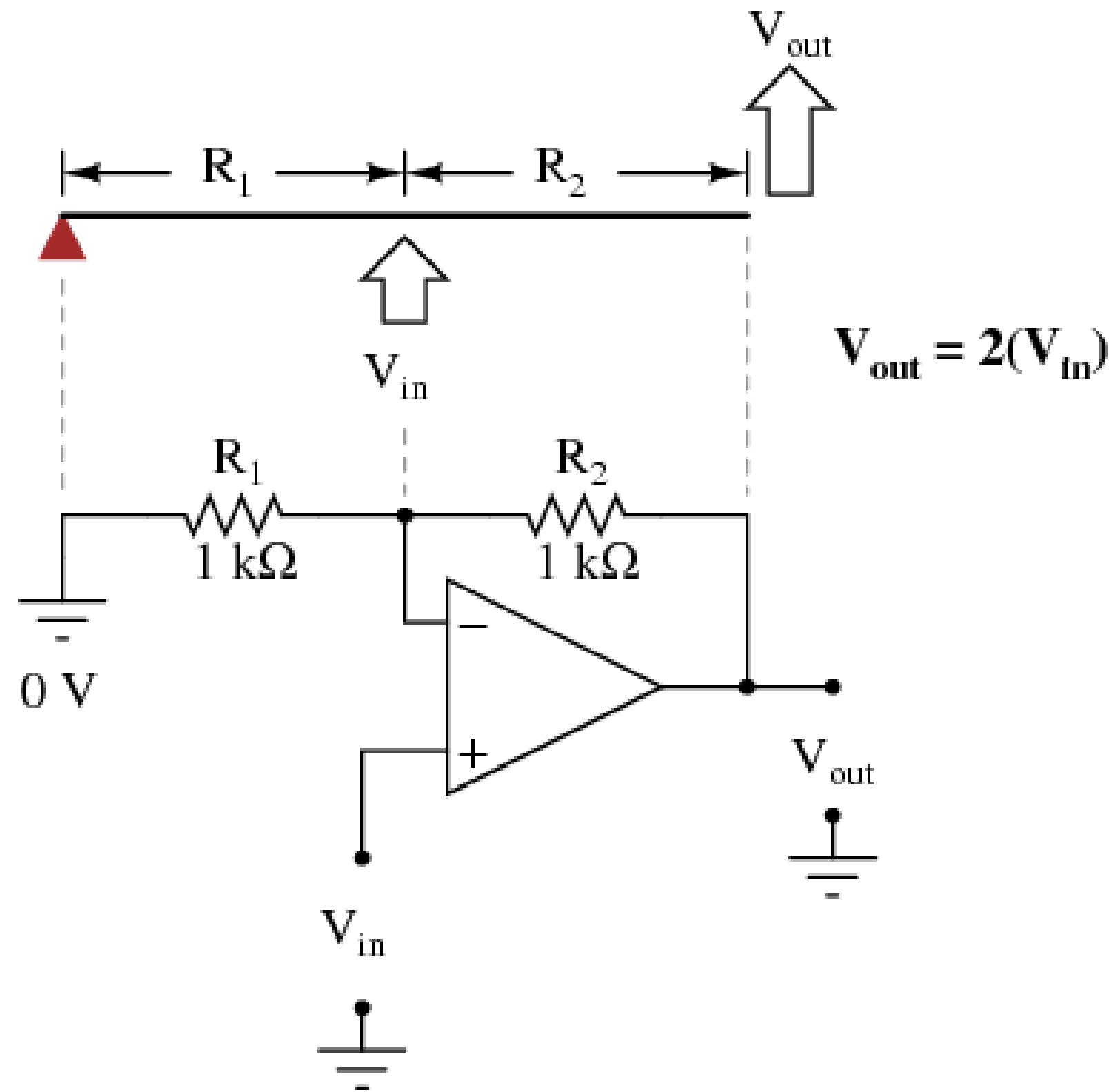
Similarity of Non-Inverting Amplifier to a Lever



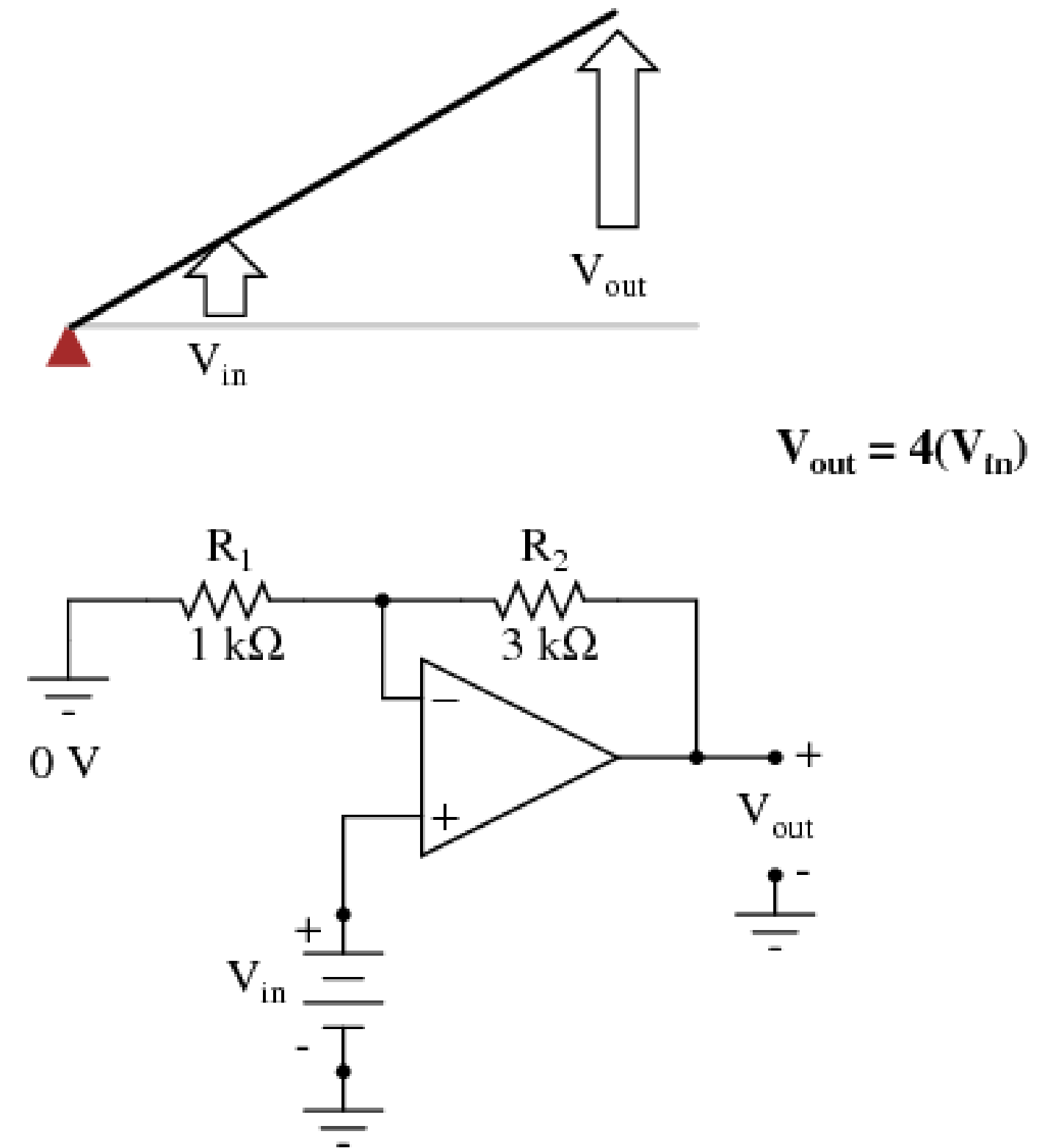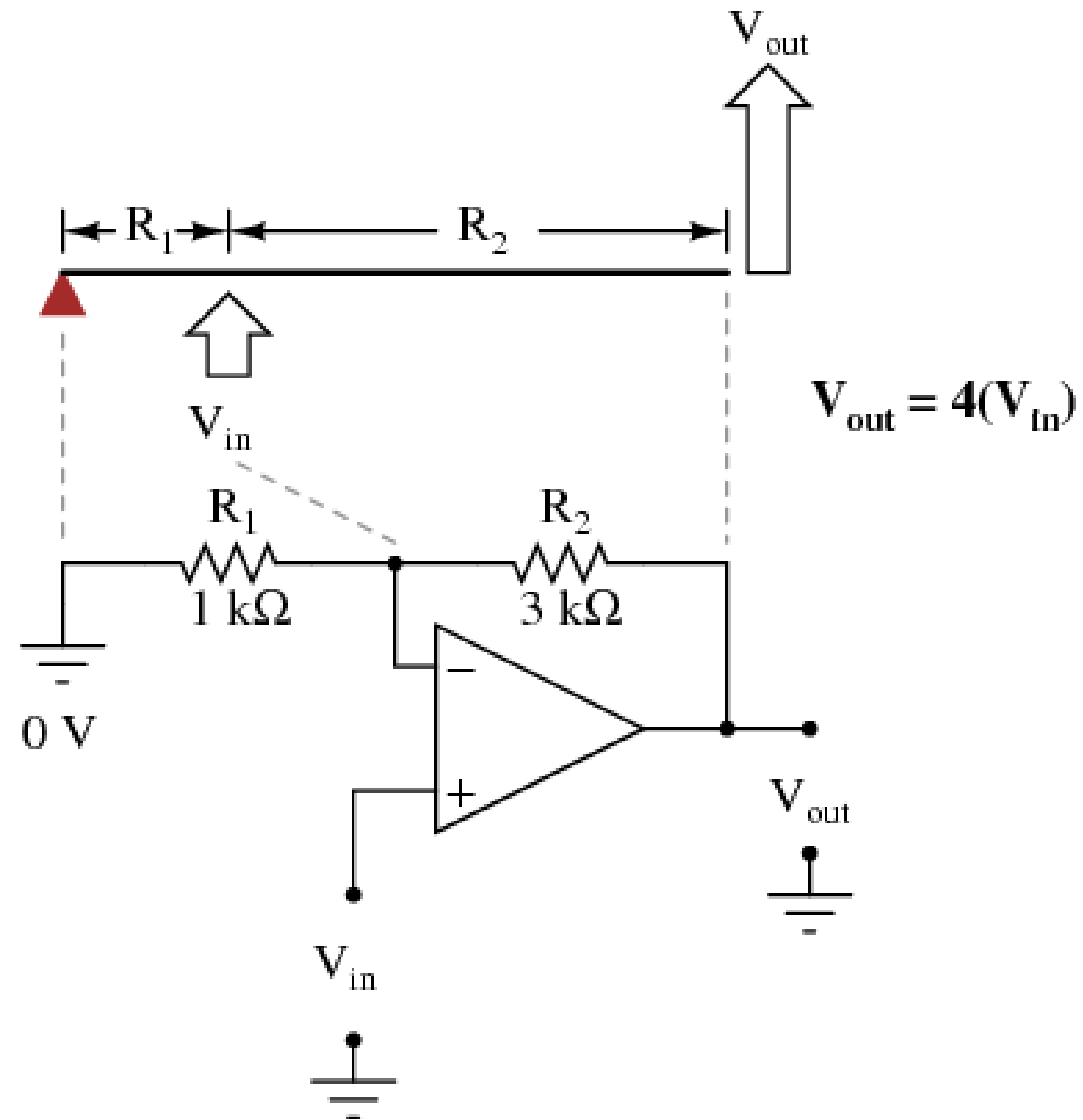Similarity of Non-Inverting Amplifier to a Lever




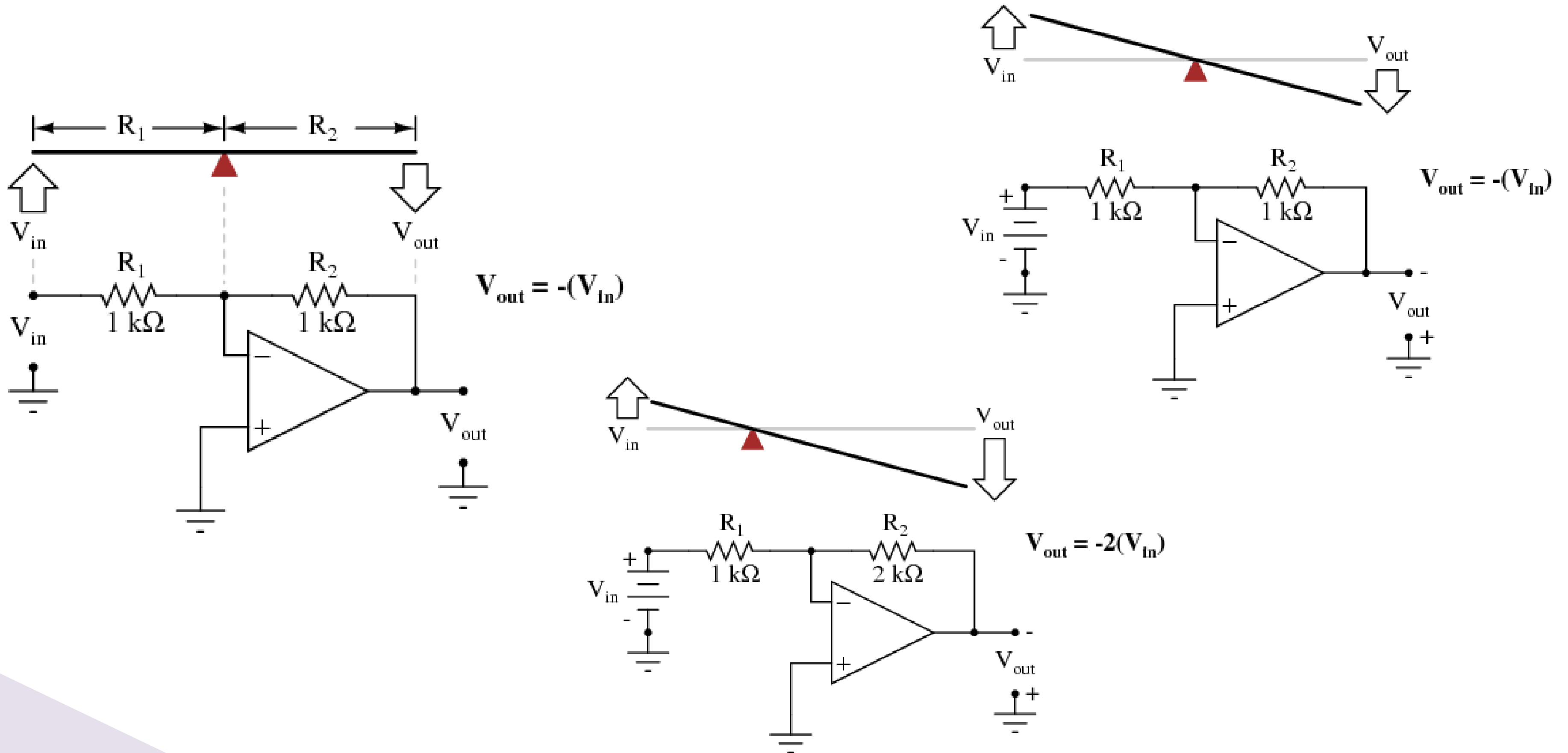Similarity of Inverting Amplifier to a Lever




Class Exercise 1

$$V_1 = ?$$

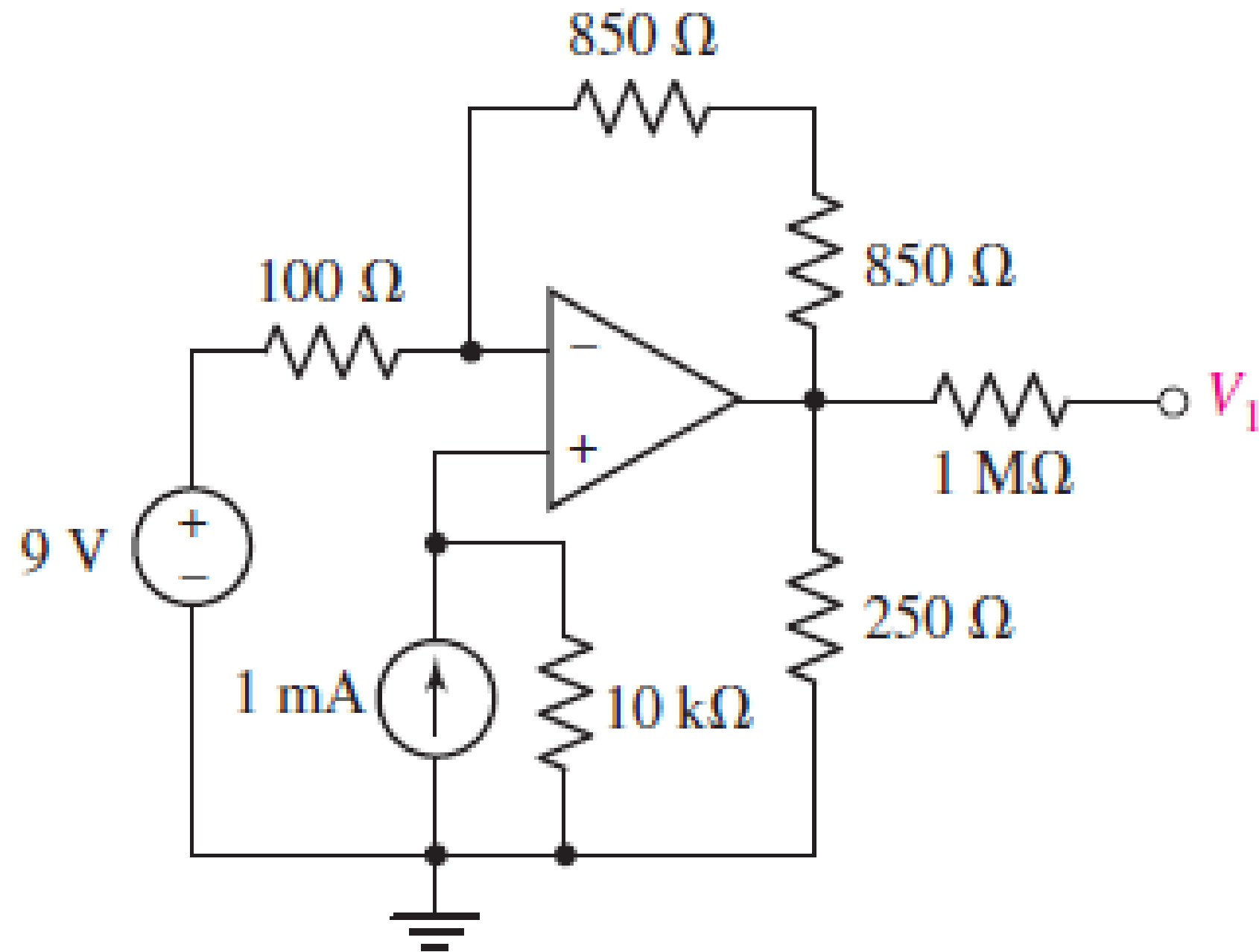


Class Exercise 2

$V_{out} = ?$

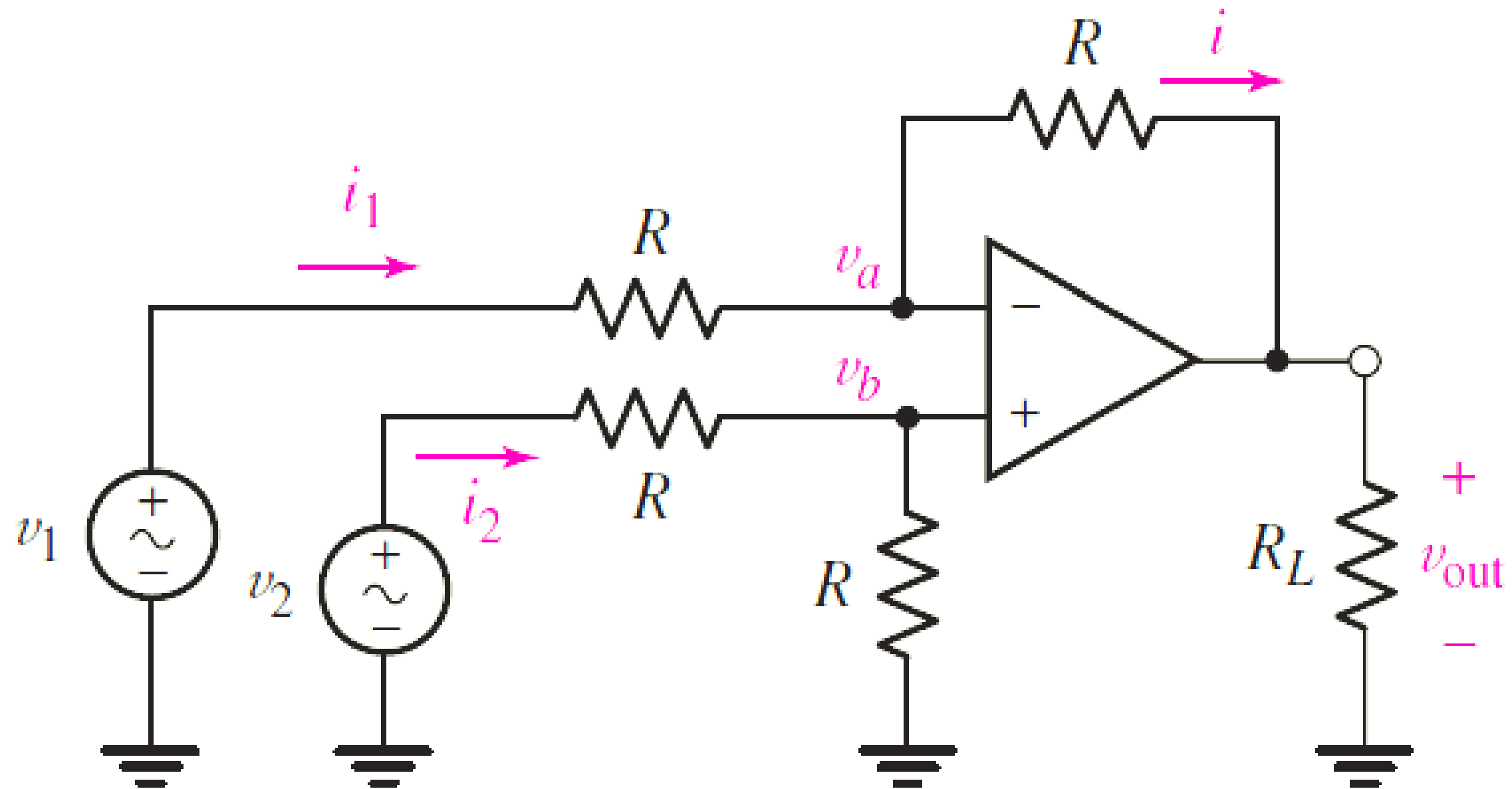

Class Exercise 3


$V_{out} = ?$

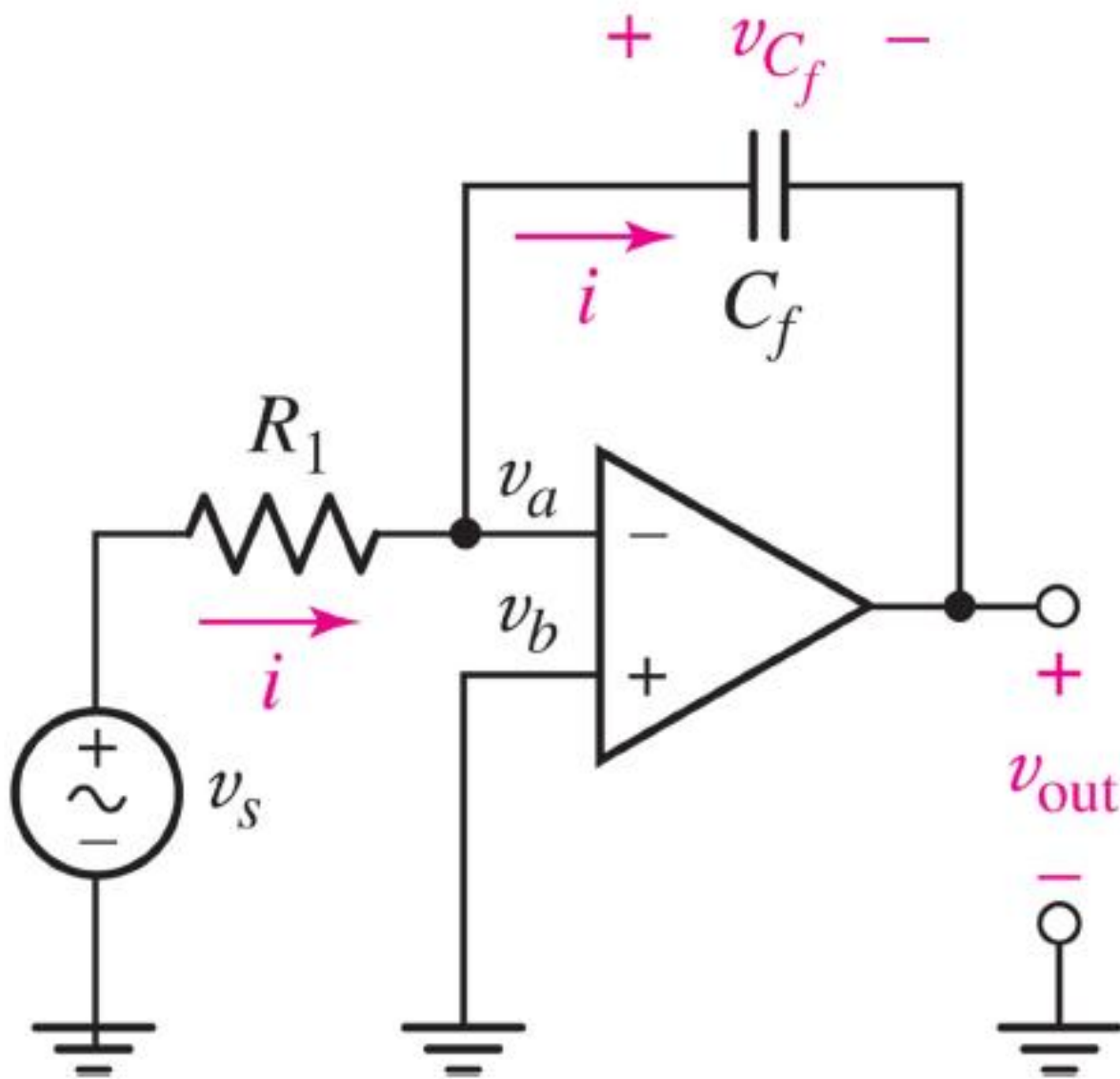

$$v_{out} = -\frac{1}{R_1 C_f} \int_0^t v_s dt' - v_{C_f}(0)$$

Class Exercise 4


$V_{out} = ?$

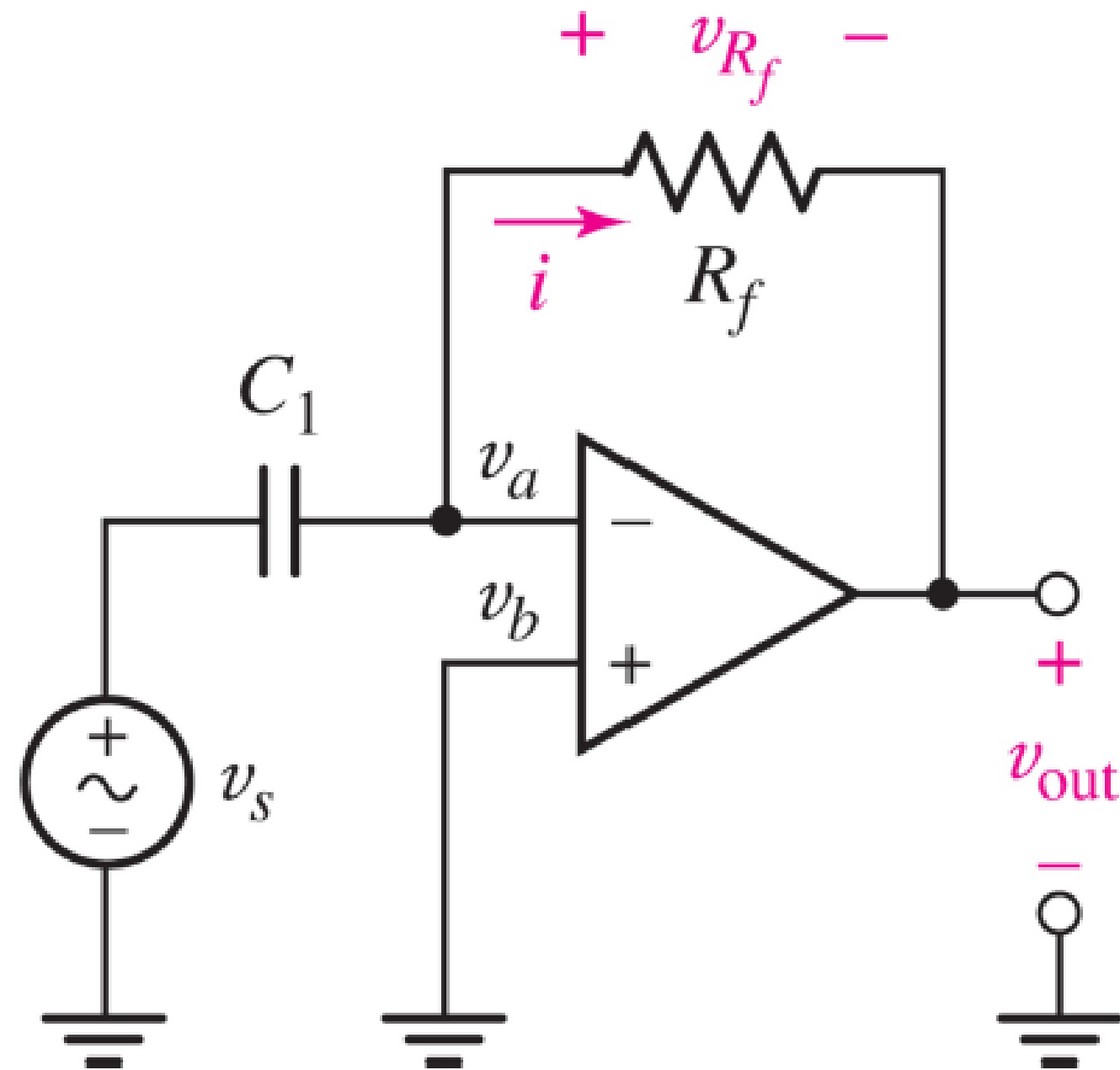

$$v_{out} = -C_1 R_f \frac{dv_s}{dt}$$


Class Exercise 5

$$v_x = ?$$

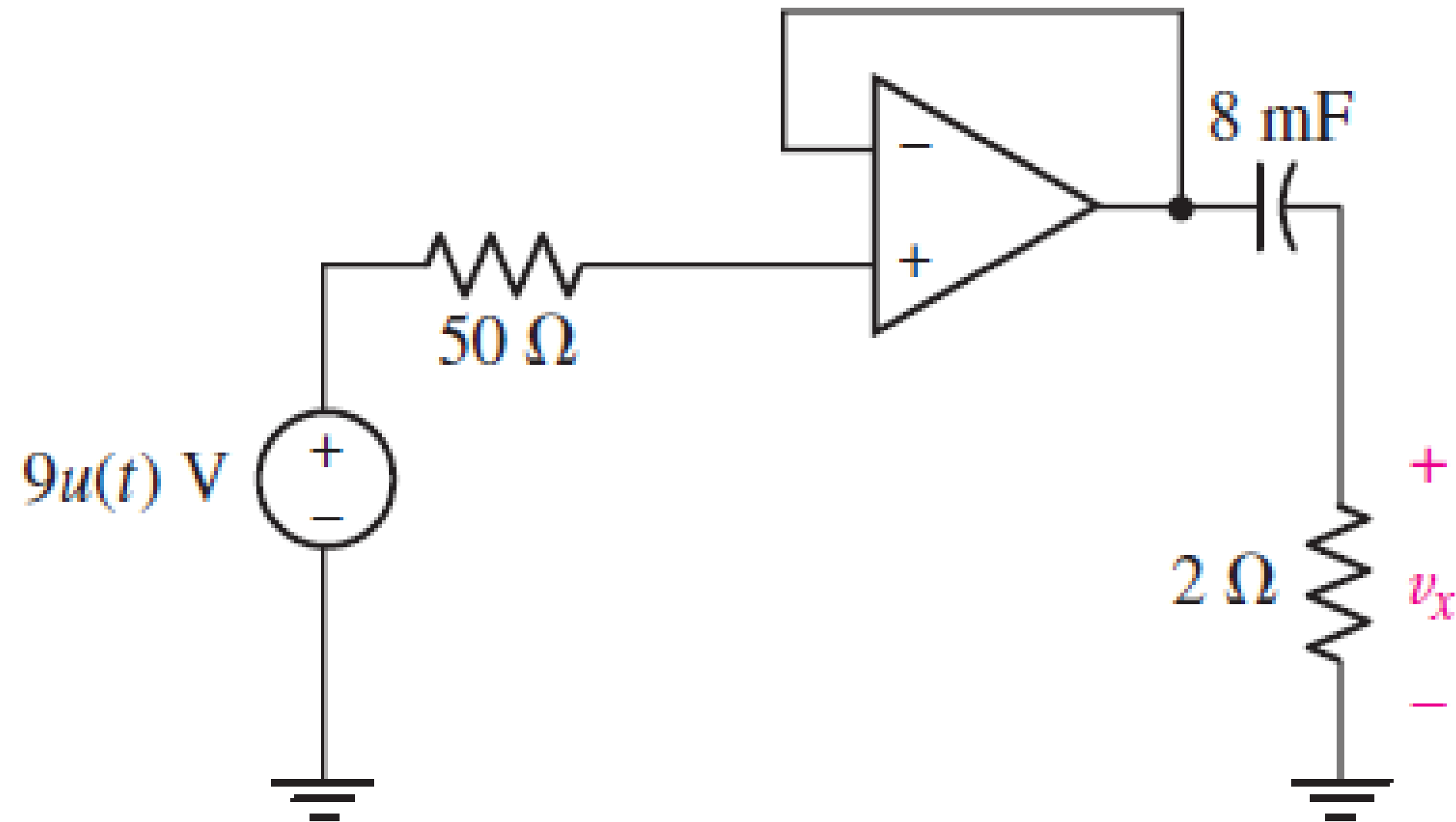

Class Exercise 6

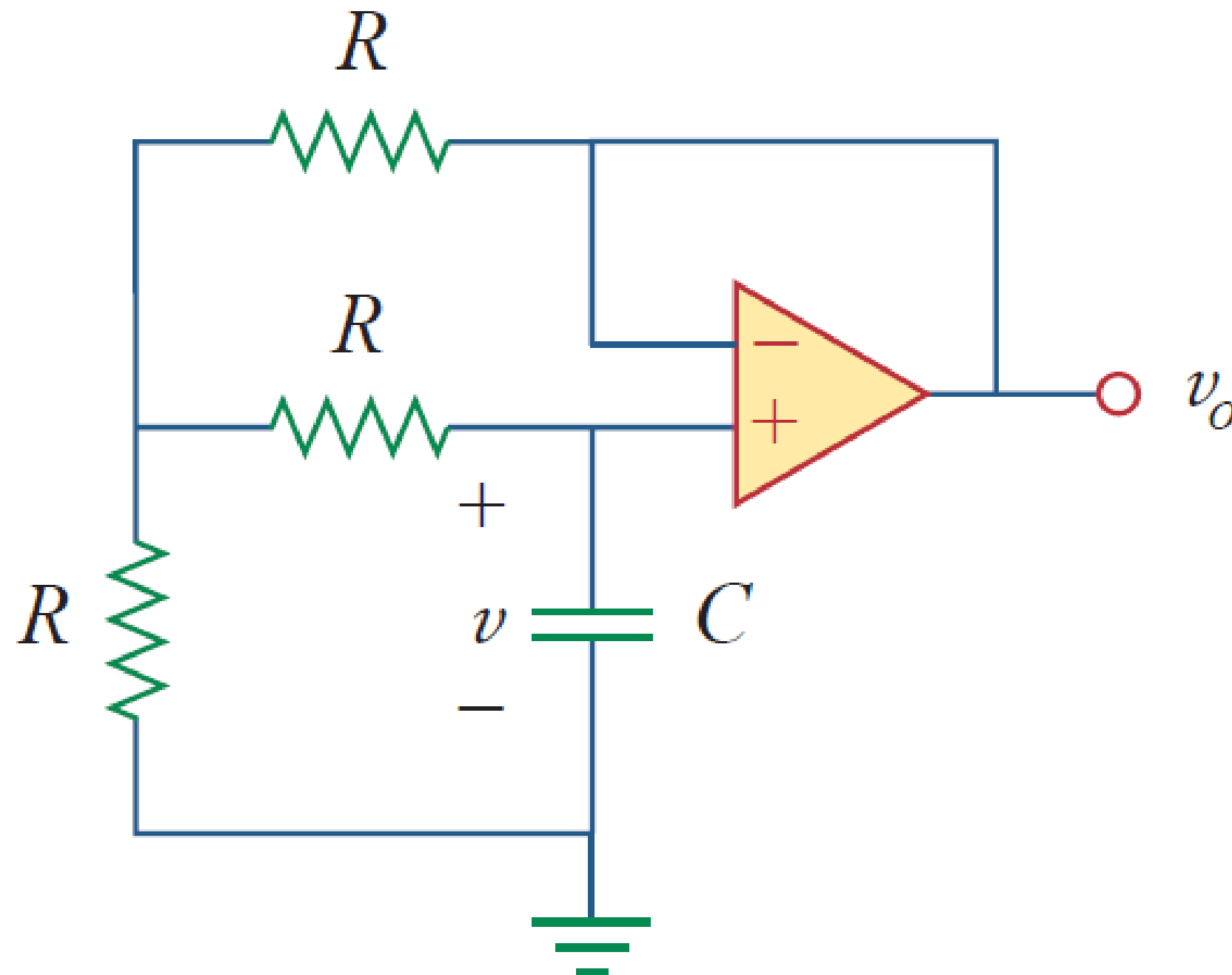
If the initial voltage across the capacitor at time $t = 0$ is 10 volts, determine the output voltage v_o .



Class Exercise 7


➤ $v_s = 10u(t)mV$, $R_1 = R_2 = 10K\Omega$, $C_1 = 20\mu F$, $C_2 = 100\mu F$

➤ $v_o = ?$

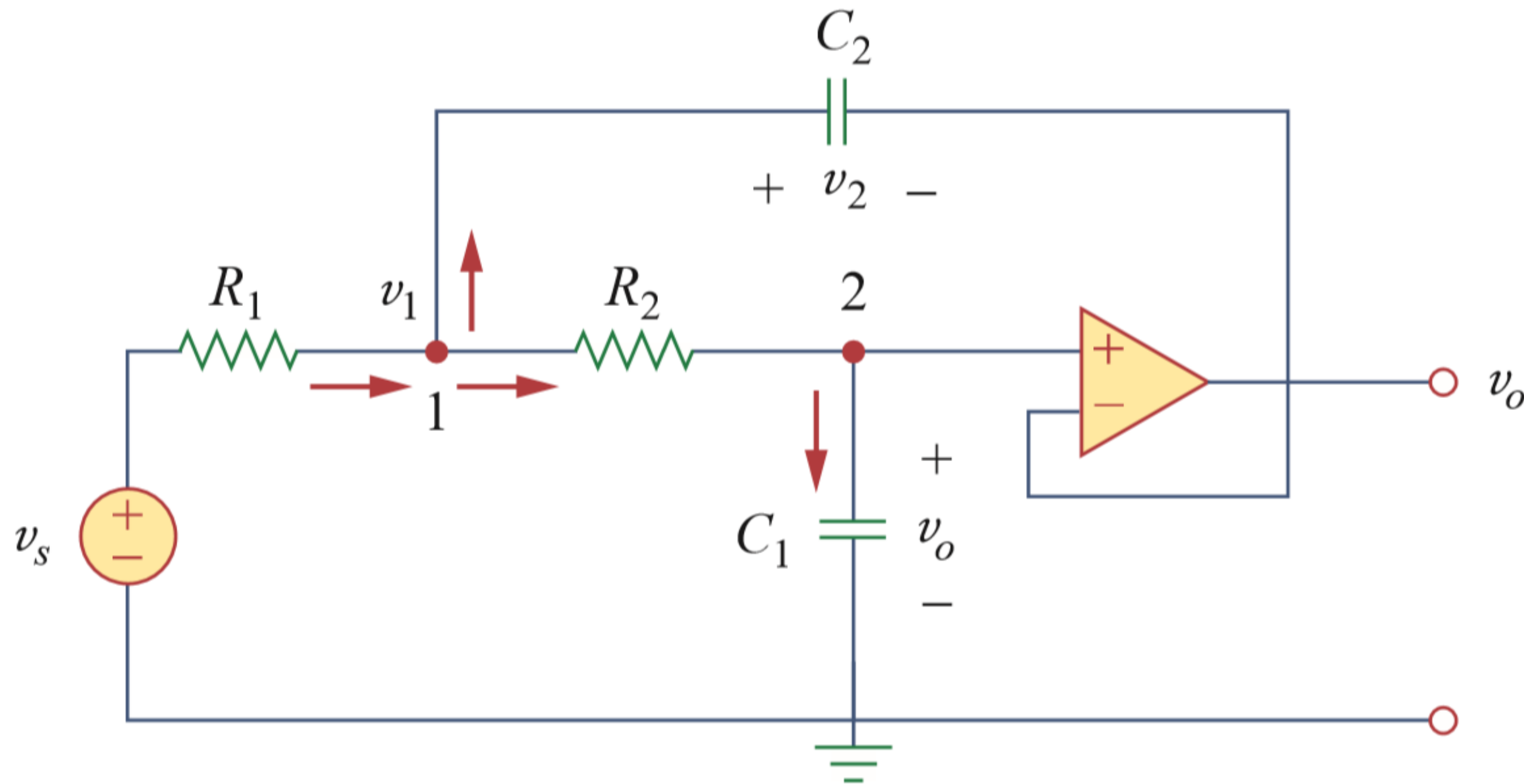


Class Exercise 8

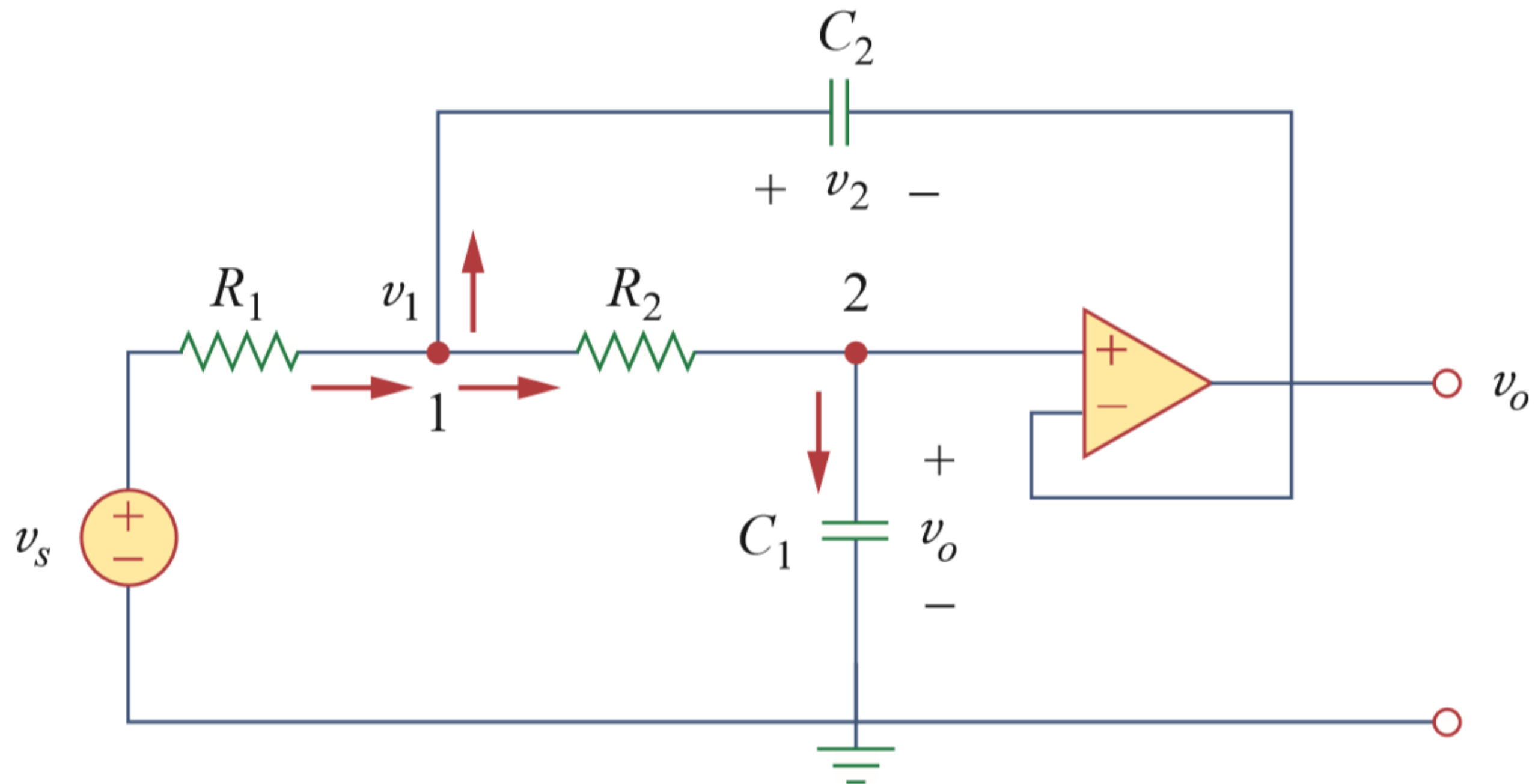- $v_s = \cos(t)mV$, $R_1 = R_2 = 10K\Omega$, $C_1 = 20\mu F$, $C_2 = 100\mu F$
- $v_o = ?$ (Use phasors).




Class Exercise 9

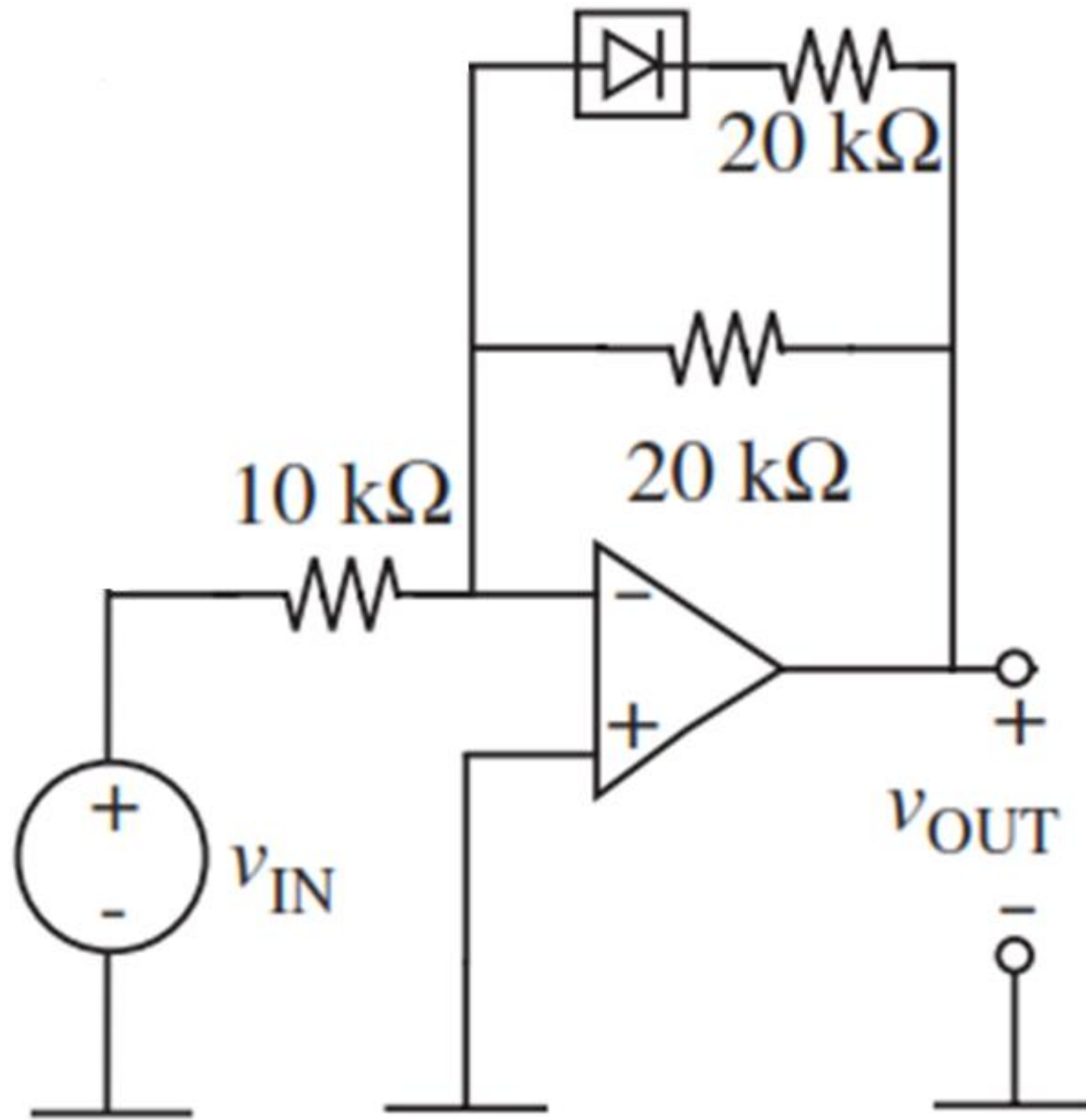If $v_{in} = \sin(200\pi t)$, plot the output voltage v_{out} .




Class Exercise 10

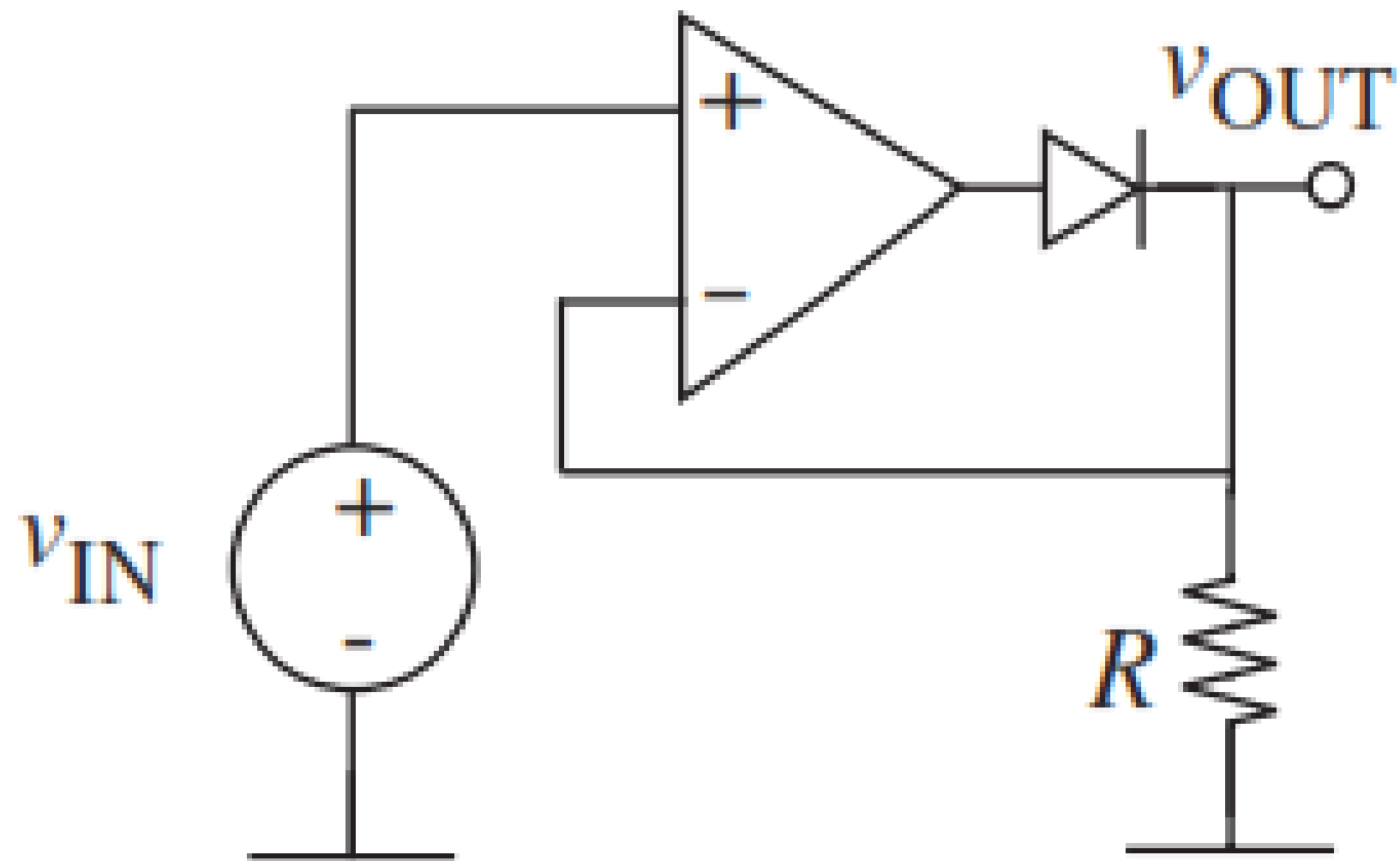- Plot the diagram of v_{out} as a function of v_{in} .



Class Exercise 11

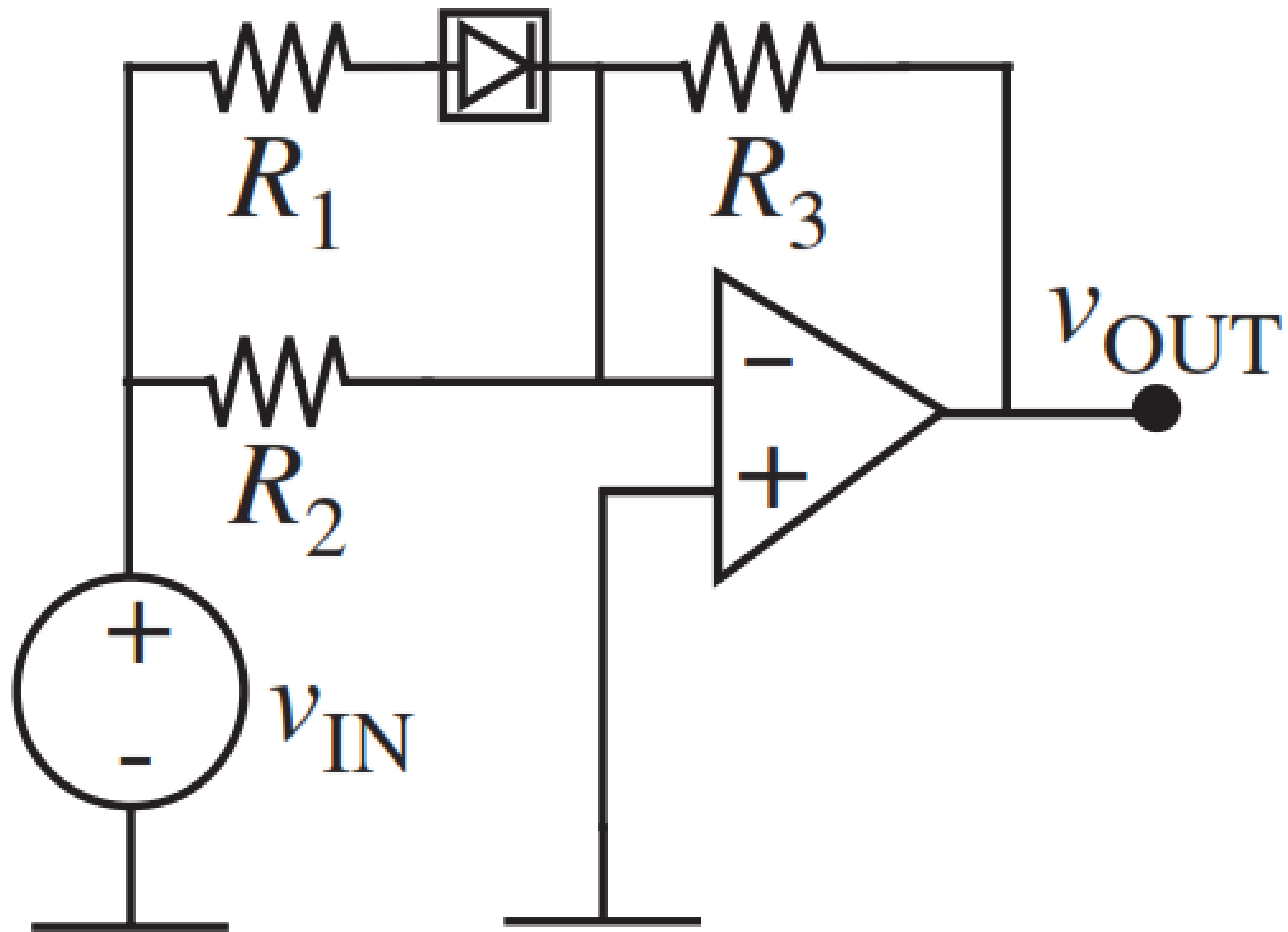
- Plot the diagram of v_{out} as a function of v_{in} .



Class Exercise

This is an active filter (using an op-amp in a frequency filter). Calculate:

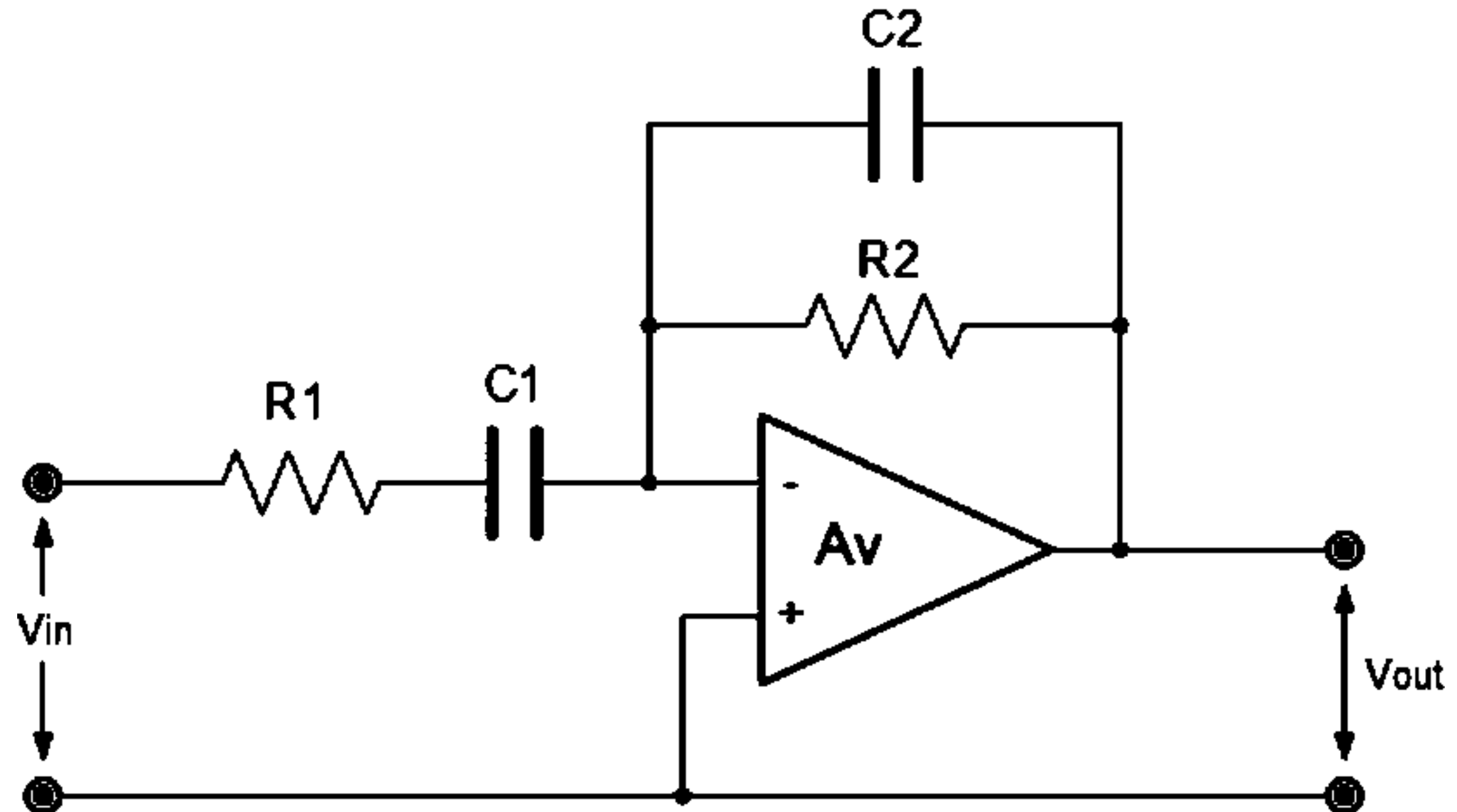- ✓ The type of filter
- ✓ The filter gain
- ✓ The cut-off frequency





Thanks
